

Course Title:	Computer Organization and Architecture
Course Number:	COE608
Semester/Year (e.g.F2016)	W2025

Instructor:	Demetres Kostas
--------------------	-----------------

<i>Assignment/Lab Number:</i>	Lab 6
<i>Assignment/Lab Title:</i>	The Complete CPU (Overall Project)

<i>Submission Date:</i>	Apr 2, 2025
<i>Due Date:</i>	Apr 9, 2025

Student LAST Name	Student FIRST Name	Student Number	Section	Signature*
Qureshi	Maheen	[REDACTED]	[REDACTED]	[REDACTED]

*By signing above you attest that you have contributed to this written lab report and confirm that all work you have contributed to this lab report is your own work. Any suspicion of copying or plagiarism in this work will result in an investigation of Academic Misconduct and may result in a “0” on the work, an “F” in the course, or possibly more severe penalties, as well as a Disciplinary Notice on your academic record under the Student Code of Academic Conduct, which can be found online at:

<https://www.torontomu.ca/content/dam/senate/policies/pol60.pdf>

Part I - CPU Reset Circuitry

1. VHDL Implementation

Reset Circuit

```

1  LIBRARY ieee;
2  USE ieee.std_logic_1164.ALL;
3  USE ieee.std_logic_arith.ALL;
4  USE ieee.std_logic_unsigned.ALL;
5
6  ENTITY reset_circuit IS
7      PORT
8      (
9          Reset:      IN STD_LOGIC;
10         Clk:        IN STD_LOGIC;
11         Enable_PD:  OUT STD_LOGIC := '1';
12         Clr_PC:     OUT STD_LOGIC
13     );
14 END reset_circuit;
15
16 ARCHITECTURE Behavior OF reset_circuit IS
17     TYPE clkNum IS (clk0,clk1,clk2,clk3);
18     SIGNAL present_clk: clkNum;
19 BEGIN
20     process(Clk)begin
21         if rising_edge(Clk) then
22             if Reset = '1' then
23                 Clr_PC <= '1';
24                 Enable_PD <= '0';
25                 present_clk <= clk0;
26             elsif present_clk <= clk0 then
27                 present_clk <= clk1;
28             elsif present_clk <= clk1 then
29                 present_clk <= clk2;
30             elsif present_clk <= clk2 then
31                 present_clk <= clk3;
32             elsif present_clk <= clk3 then
33                 Clr_PC <= '0';
34                 Enable_PD <= '1';
35             end if;
36         end if;
37     end process;
38 END Behavior;
39

```

Figure 1.0: VHDL code from reset_circuit.vhd

[Figure 1.0](#) Represents the code used to reset the circuit. With the inputs being Reset and Clk, and the outputs being Enable_PD and Clr_PC. Essentially, when the reset is equal to 1, then the PC is reset.

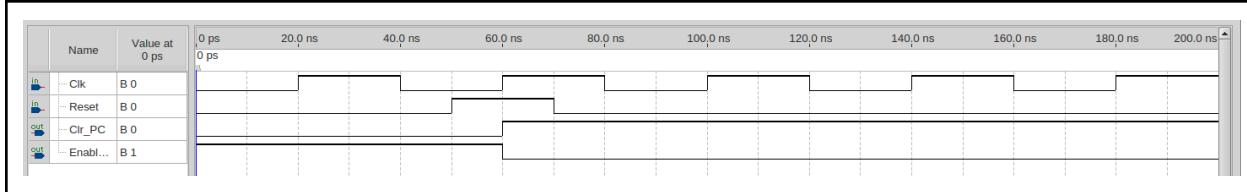


Figure 1.1: Waveform from reset_circuit.vwf

Figure 1.1 This waveform shows how the reset circuit functions. It is visible that until Reset is raised to 1, the Clr_PC is

Upper Zero Value Extender


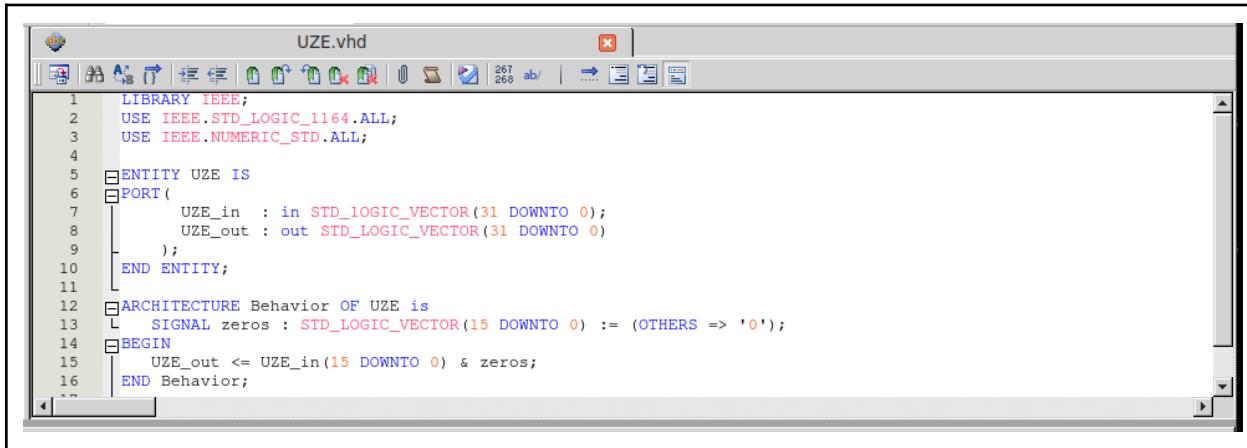


Figure 1.2: VHDL code from UZE.vhd

The UZE.vhd file in [Figure 1.2](#) represents an Upper Zero Value Extender, which takes the lower 16 bits (15 to 0) and stores them as the upper 16 bits (31 to 16), while replacing the rest with zero. This is often used in scenarios that require LSB of the Instruction Register (IR) to be the MSB (31 to 16) of the destination. Within the code, the ports consist of a 32 bit input and output named UZE_IN and UZE_OUT respectively. The architecture is very simple and consists of replacing the upper byte (32 to 16 bits) with the last 16 bits (15 to 0) of the input, and replacing the last 15 to 0 bits of the output UZE_OUT with zeros, which is then output through UZE_OUT.

32-Bit Register

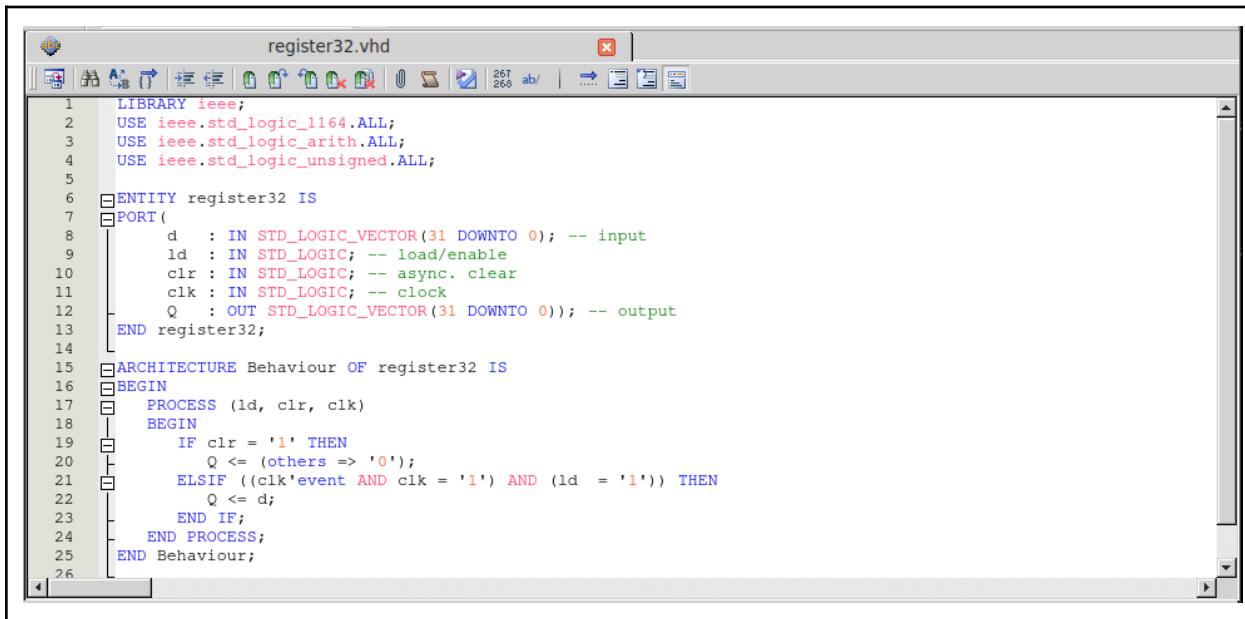

```


1 LIBRARY ieee;
2 USE ieee.std_logic_1164.ALL;
3 USE ieee.std_logic_arith.ALL;
4 USE ieee.std_logic_unsigned.ALL;
5
6 ENTITY register32 IS
7 PORT(
8     d : IN STD_LOGIC_VECTOR(31 DOWNTO 0); -- input
9     ld : IN STD_LOGIC; -- load-enable
10    clr : IN STD_LOGIC; -- async. clear
11    clk : IN STD_LOGIC; -- clock
12    Q : OUT STD_LOGIC_VECTOR(31 DOWNTO 0)); -- output
13 END register32;
14
15 ARCHITECTURE Behaviour OF register32 IS
16 BEGIN
17 BEGIN
18     PROCESS (ld, clr, clk)
19     BEGIN
20         IF clr = '1' THEN
21             Q <= (others => '0');
22         ELSIF ((clk'event AND clk = '1') AND (ld = '1')) THEN
23             Q <= d;
24         END IF;
25     END PROCESS;
26 END Behaviour;

```

Figure 1.3: VHDL code from register32.vhd

Figure 1.3 depicts the VHDL code for a 32-bit register. The code first establishes the various ports of the register, such as inputs d (data) with 32-bit storage, ld (load-enable), clr (clear), clk (clock) and output Q with 32-bit storage. In terms of functionality of the register, during a rising edge clock (clk = '1') and load (ld = '1'), all 32 bits of data (d) is stored into all 32 bits of the output (Q). The VHDL code also establishes the functionality of the clear input within the register, where its rising edge (clr = '1') clears all 32 bits of output (Q) to zero.

Reducer Unit

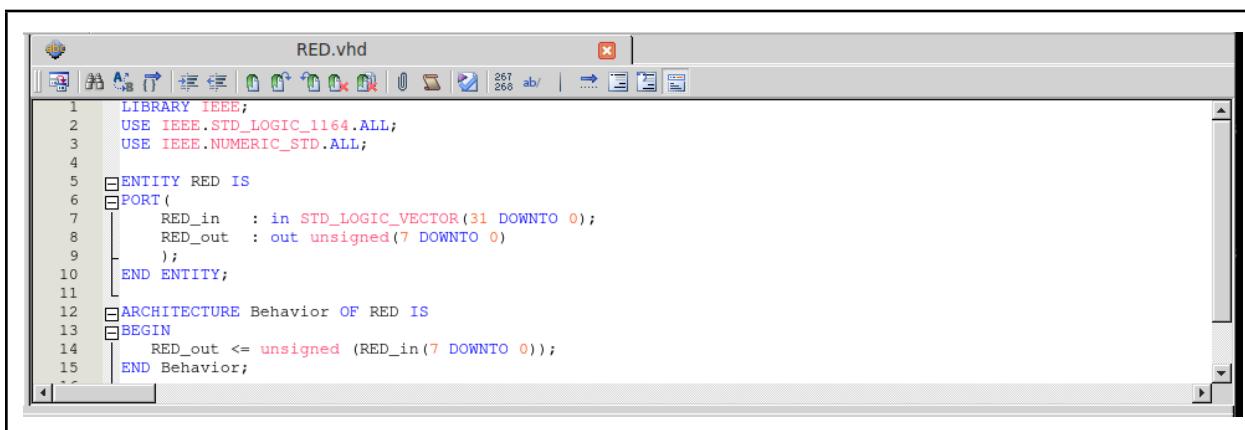

```

1 LIBRARY IEEE;
2 USE IEEE.STD_LOGIC_1164.ALL;
3 USE IEEE.NUMERIC_STD.ALL;
4
5 ENTITY RED IS
6 PORT(
7     RED_in : in STD_LOGIC_VECTOR(31 DOWNTO 0);
8     RED_out : out unsigned(7 DOWNTO 0)
9 );
10 END ENTITY;
11
12 ARCHITECTURE Behavior OF RED IS
13 BEGIN
14     RED_out <= unsigned (RED_in(7 DOWNTO 0));
15 END Behavior;

```

Figure 1.4: VHDL code from RED.vhd

The RED.vhd file in Figure 1.4 represents a Reducer Unit, which is in charge of performing reduction operations on the signal. It takes the 32-bit input, and outputs 8-bit. It continues on by essentially extracting the lower 8-bits out of the 32-bit input in the ARCHITECTURE.

4-to-1 Multiplexer

```

1 LIBRARY IEEE;
2 USE IEEE.STD_LOGIC_1164.ALL;
3
4 ENTITY mux4to1 IS
5 PORT ( s : in STD_LOGIC_VECTOR(1 DOWNTO 0);
6 X1, X2, X3, X4 : in STD_LOGIC_VECTOR (31 DOWNTO 0);
7 f : out STD_LOGIC_VECTOR(31 DOWNTO 0));
8 END mux4to1;
9
10 ARCHITECTURE Behavior OF mux4to1 IS
11 BEGIN
12 WITH s SELECT
13 f <= X1 when "00",
14 X2 when "01",
15 X3 when "10",
16 X4 when "11";
17 END Behavior;

```

Figure 1.5: VHDL code from mux4to1.vhd

[Figure 1.5](#) depicts the 4 to 1 Multiplexer included in the data processor. Taking 4 inputs, it assigns certain 2-bit values from 0 to 3 to each of the input values and provides a single output, f.

2-to-1 Multiplexer

```

1 LIBRARY ieee;
2 USE ieee.std_logic_1164.ALL;
3 USE ieee.std_logic_arith.ALL;
4 USE ieee.std_logic_unsigned.ALL;
5
6 ENTITY mux2to1 IS
7 PORT ( s : IN std_logic;
8 w0, w1 : IN std_logic_vector(31 DOWNTO 0);
9 f : OUT std_logic_vector(31 DOWNTO 0));
10 END mux2to1;
11
12 ARCHITECTURE Behaviour of mux2to1 IS
13 BEGIN
14 WITH s SELECT
15 f <= w0 when '0',
16 w1 when others;
17 END Behaviour;

```

Figure 1.6: VHDL code from mux2to1.vhd

[Figure 1.6](#) depicts the VHDL code for a 2-to-1 multiplexer that is also used within the program counter below. The role of the multiplexer is to output a specific value of one of the inputs based on a selection.

The inputs of the 2-to-1 multiplexer are the selection input (s), input 0 (w0) and input 1 (w1) of the multiplexer and the output function (f). Within the behaviour of the 2-to-1 multiplexer, the function (f) outputs the 32-bit input 0 (w0) when the selector is '0' and the 32-bit input 1 (w1) when the selector is '1'.

Lower Value Zero Extender

```

1 LIBRARY IEEE;
2 USE IEEE.STD_LOGIC_1164.ALL;
3 USE IEEE.NUMERIC_STD.ALL;
4
5 ENTITY LZE IS
6 PORT( LZE_IN : in STD_LOGIC_VECTOR(31 DOWNTO 0);
7       LZE_OUT : out STD_LOGIC_VECTOR(31 DOWNTO 0)
8       );
9 END ENTITY;
10
11 ARCHITECTURE Behaviour OF LZE IS
12 SIGNAL zeros: STD_LOGIC_VECTOR(15 DOWNTO 0) := (others => '0');
13 BEGIN
14   LZE_out <= zeros & LZE_in(15 DOWNTO 0);
15 END Behaviour;

```

Figure 1.7: VHDL code from LZE.vhd

The LZE.vhd file in [Figure 1.7](#) represents a Lower Zero Value Extender, which sets the higher bits (31 to 16) to 0 and the lower half (15 to 0) as its original inputs. These are used for immediate operations and loading addresses as witnessed within the LUI (Load Upper Immediate) waveform, as the lower 16 bits of the Instruction Register (IR) are loaded to Register A. It is also used in ADDI (Add Immediate) and ORI (Or Immediate) operations, where the Instruction Register (IR) that holds the lower 16 bits is used as the second operand. Within the code, the ports consist of a 32 bit input and output named LZE_IN and LZE_OUT respectively. The architecture is very simple and consists of replacing the upper byte (32 to 16 bits) with zeros and keeping the last 16 bits (15 to 0) as the input, which is then output through LZE_OUT.

1-Bit Full Adder

```


1 library ieee;
2 use ieee.std_logic_1164.all;
3
4 entity fulladd is
5 port(
6   Cin, x, y : in std_logic;
7   s, Cout : out std_logic
8 );
9 end fulladd;
10
11 architecture Behaviour of fulladd is
12 begin
13   s <= x xor y xor Cin;
14   Cout <= (x and y) or (Cin and x) or (Cin and y);
15 end Behaviour;

```

Figure 1.8: VHDL code from fulladd.vhd

[Figure 1.8](#) depicts a 1-Bit Full Adder in VHDL code. The code establishes the functionality of a 1-Bit Full Adder through distinguishing the various ports that compose the component's inputs Cin (Carry in), x and y, as well as outputs s (sum) and Cout (Carry out). The behaviours of outputs s and Cout are defined within the architecture, where s (sum) equates to the xorring of the three inputs x, y and Cin ($x \oplus y \oplus \text{Cin}$). As for Cout, the three inputs are anded and or-ed with one another ((x AND y) OR (Cin AND x) OR (Cin AND y)).

Memory Module Design

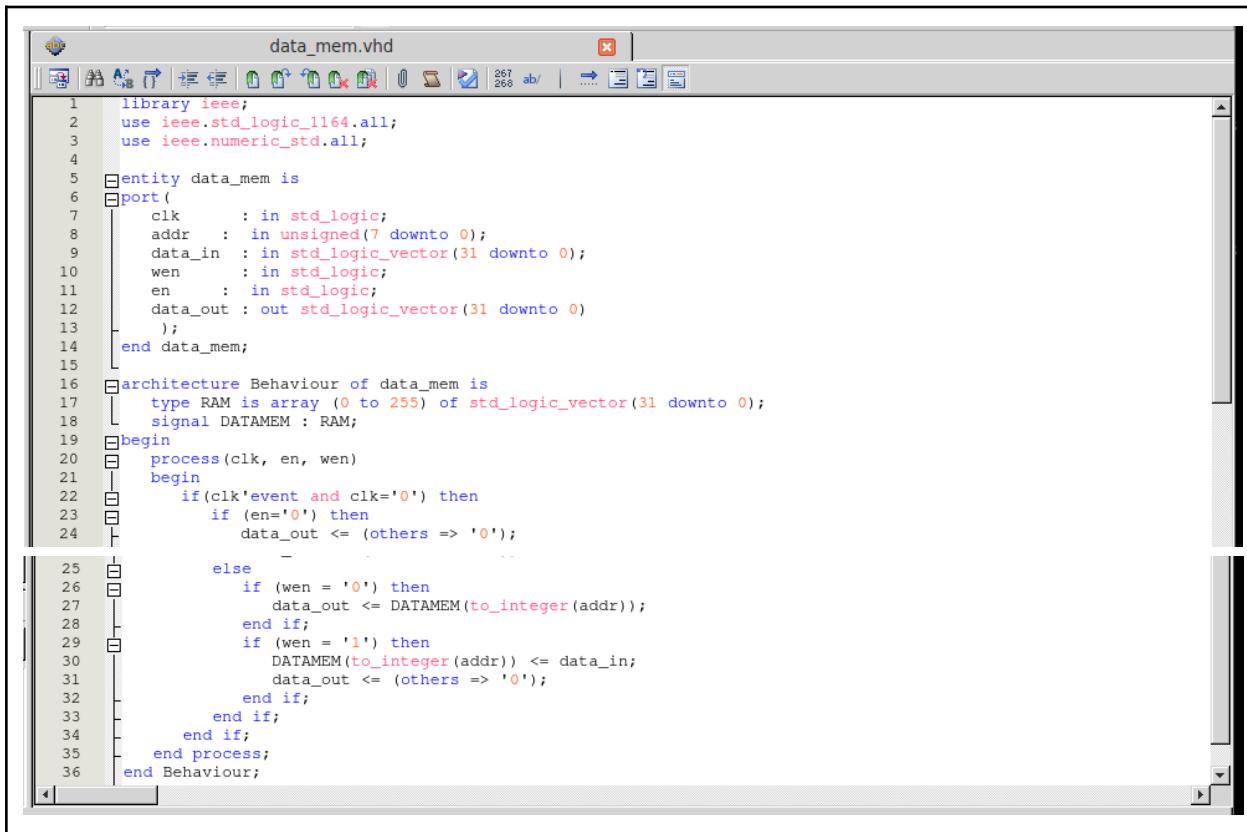

```

1 library ieee;
2 use ieee.std_logic_1164.all;
3 use ieee.numeric_std.all;
4
5 entity data_mem is
6 port(
7     clk      : in std_logic;
8     addr    : in unsigned(7 downto 0);
9     data_in : in std_logic_vector(31 downto 0);
10    wen     : in std_logic;
11    en      : in std_logic;
12    data_out : out std_logic_vector(31 downto 0)
13 );
14 end data_mem;
15
16 architecture Behaviour of data_mem is
17 type RAM is array (0 to 255) of std_logic_vector(31 downto 0);
18 signal DATAMEM : RAM;
19 begin
20 process(clk, en, wen)
21 begin
22 if(clk'event and clk='0') then
23 if (en='0') then
24     data_out <= (others => '0');
25 else
26     if (wen = '0') then
27         data_out <= DATAMEM(to_integer(addr));
28     end if;
29     if (wen = '1') then
30         DATAMEM(to_integer(addr)) <= data_in;
31         data_out <= (others => '0');
32     end if;
33 end if;
34 end if;
35 end process;
36 end Behaviour;

```

Figure 1.9: VHDL code from data_mem.vhd

The data_mem.vhd file in [Figure 1.9](#) represents a memory module designed to read and write data within a clock cycle. The various ports within the memory unit assist in carrying out the functionality of the unit. This includes inputs clk (clock), addr (8-bit address input), data_in (32-bit data input), wen (32-bit write enable), en (enable), and output data_out (32-bit data output). Within the behaviour of the object, a RAM type array can store the assigned value of data_in when en = 1 and wen = 1 at the assigned value of addr during a falling edge of the input clock. As for reading data, it requires en = 1 and wen = 0, which will return the data stored at the assigned value of addr to data_out during a falling-edge of a clock cycle.

When en = 0, regardless of any other inputs or clock edge, there will be no functionality.

Arithmetic Logic Unit (ALU)

```

library ieee;
use ieee.std_logic_1164.all;
use ieee.std_logic_arith.all;
use ieee.std_logic_unsigned.all;
use ieee.numeric_std.all;
entity alu is
port(
    a : in std_logic_vector(31 downto 0);
    b : in std_logic_vector(31 downto 0);
    op : in std_logic_vector(2 downto 0);
    result : out std_logic_vector(31 downto 0);
    zero : out std_logic;
    cout : out std_logic
);
end alu;
architecture Behavior of alu is
component adder32
port(
    Cin : in std_logic;
    X,Y : in std_logic_vector(31 downto 0);
    S : out std_logic_vector(31 downto 0);
    Cout : out std_logic
);
end component;
signal result_s: std_logic_vector(31 downto 0):= (others => '0');
signal result_add: std_logic_vector(31 downto 0):= (others => '0');
signal result_sub: std_logic_vector(31 downto 0):= (others => '0');
signal cout_s : std_logic := '0';
signal cout_add : std_logic := '0';
signal cout_sub : std_logic := '0';
signal zero_s : std_logic;
begin
    add0 : adder32 port map (op(2),a,b,result_add, cout_add);
    sub0 : adder32 port map (op(2), a, not b, result_sub, cout_sub);
process (a, b, op)
begin
    case (op) is
        when "000" =>
            result_s <= a and b;
            cout_s <= '0';

        when "001" =>
            result_s <= a or b;
            cout_s <= '0';
        when "010" =>
            result_s <= result_add;
            cout_s <= cout_add;
        when "011" =>
            result_s <= b;
            cout_s <= '0';
        when "110" =>
            result_s <= result_sub;
            cout_s <= cout_sub;
        when "100" =>
            result_s <= a(30 downto 0) & '0';
            cout_s <= a(31);
        when "101" =>
            result_s <= '0' & a(31 downto 1);
            cout_s <= '0';
        when others =>
            result_s <= a;
            cout_s <= '0';
    end case;
    case (result_s) is
        when (others => '0') =>
            zero_s <= '1';
        when others =>
            zero_s <= '0';
    end case;
end process;
result <= result_s;
cout <= cout_s;
zero <= zero_s;
end Behavior;

```

Figure 1.10: VHDL code from alu.vhd

Figure 3.4 represents the code for the 32-bit ALU. This consists of three main inputs (a, b and op) and three outputs (result, zero and cout). It is necessary to incorporate the previously created 32-bit adder so as to complete calculations for this component. All signals are output using ‘signal result’, and ‘port map’ is utilised to connect all of these input ports to the output ports. It is necessary to be able to handle cases for all possible binary values for op, which is represented in process(a,b,op). Different values result in cout_s giving the correct respective outputs for the ALU. As there are two ports for zero_s, the cases of it being equivalent to ‘0’ or ‘1’ are handled, and the output for cout and result conclude the code.

32-Bit Adder

```

library ieee;
use ieee.std_logic_1164.all;

entity adder32 is
port(
    Cin      : in std_logic;
    X,Y     : in std_logic_vector(31 downto 0);
    S        : out std_logic_vector(31 downto 0);
    Cout    : out std_logic
);
end adder32;

architecture Behaviour of adder32 is
component adder16
port(
    Cin      : in std_logic;
    X,Y     : in std_logic_vector(15 downto 0);
    S        : out std_logic_vector(15 downto 0);
    Cout    : out std_logic
);
end component;
begin
    signal C : std_logic;
begin
    stage0: adder16 port map (Cin, X(15 downto 0), Y(15 downto 0), S(15 downto 0), C);
    stage1: adder16 port map (C, X(31 downto 16), Y(31 downto 16), S(31 downto 16), Cout);
end Behaviour;

```

Figure 1.11: VHDL code from adder32.vhd

Figure 1.11 depicts a 32-Bit Adder/Subtractor in VHDL code. The code establishes the functionality of a 32-Bit Adder/Subtractor. The code distinguishes the various ports that compose the component's inputs

Cin (Carry in), X[31..0] and Y[31..0], as well as outputs S[31..0] (Sum) and Cout (Carry out). The behaviour of the 32-Bit Adder/Subtractor uses the 16-Bit Full Adder in 2 port maps, with specific inputs to represent the 32 bits as established in the code

16-Bit Adder

```

library ieee;
use ieee.std_logic_1164.all;

entity adder16 is
port(
    Cin      : in std_logic;
    X,Y     : in std_logic_vector(15 downto 0);
    S        : out std_logic_vector(15 downto 0);
    Cout    : out std_logic
);
end adder16;

architecture Behaviour of adder16 is
component adder4
port(
    Cin      : in std_logic;
    X, Y   : in std_logic_vector(3 downto 0);
    S       : out std_logic_vector(3 downto 0);
    Cout   : out std_logic
);
end component;
begin
    signal C : std_logic_vector(1 to 3);
begin
    stage0: adder4 port map (Cin, X(3 downto 0), Y(3 downto 0), S(3 downto 0), C(1));
    stage1: adder4 port map (C(1), X(7 downto 4), Y(7 downto 4), S(7 downto 4), C(2));
    stage2: adder4 port map (C(2), X(11 downto 8), Y(11 downto 8), S(11 downto 8), C(3));
    stage3: adder4 port map (C(3), X(15 downto 12), Y(15 downto 12), S(15 downto 12), Cout);
end Behaviour;

```

Figure 1.12: VHDL code from adder16.vhd

Figure 1.12 depicts a 16-Bit Adder in VHDL code. The code establishes the functionality of a 16-Bit Adder. The code distinguishes the various ports that compose the component's inputs Cin (Carry in), X[15..0] and Y[15..0], as well as outputs S[15..0] (Sum) and Cout (Carry out). The behaviour of the 16-Bit Adder uses the 4-Bit Full Adder in 4 port maps, with specific inputs to represent the 16 bits as established in the code.

4-Bit Adder

```

library ieee;
use ieee.std_logic_1164.all;
entity adder4 is
port(
    Cin : in std_logic;
    X, Y : in std_logic_vector(3 downto 0);
    S : out std_logic_vector(3 downto 0);
    Cout : out std_logic
);
end adder4;
architecture Behaviour of adder4 is
component fulladd
port(
    Cin, x, y : in std_logic;
    s, Cout : out std_logic
);
end component;
signal C : std_logic_vector (1 to 3);
begin
    stage0: fulladd port map (Cin, X(0), Y(0), S(0), C(1));
    stage1: fulladd port map (C(1), X(1), Y(1), S(1), C(2));
    stage2: fulladd port map (C(2), X(2), Y(2), S(2), C(3));
    stage3: fulladd port map (C(3), X(3), Y(3), S(3), Cout);
end Behaviour;

```

Figure 1.13: VHDL code from adder4.vhd

Figure 1.13 depicts a 4-Bit Adder in VHDL code. The code establishes the functionality of a 4-Bit Adder through distinguishing the various ports that compose the component's inputs Cin (Carry in), X[3..0] and Y[3..0], as well as outputs S[3..0] (Sum) and Cout (Carry out). The behaviour of the 4-Bit Adder uses the Full Adder created in Figure 3.0 in 4 port maps, with specific inputs to represent the 4 bits as established in the code.

Adder

```

LIBRARY ieee;
USE ieee.std_logic_1164.ALL;
USE ieee.std_logic_arith.ALL;
USE ieee.std_logic_unsigned.ALL;
ENTITY add IS
PORT (A : IN std_logic_vector(31 DOWNTO 0);
       B : OUT std_logic_vector(31 DOWNTO 0)
      );
END add;
ARCHITECTURE Behaviour OF add IS
BEGIN
B <= A + 4;
END Behaviour;

```

Figure 1.14: VHDL code from add.vhd

Figure 1.14 depicts the VHDL code for an adder that is used for the Program Counter below. The role of the adder is to increment any 32 bit input (A) by 4, and then output it to B. Within the VHDL code add, it establishes the input (A) and output (B), and then its behaviour of setting B to the increment of A by 4.

Program Counter

```


1 LIBRARY ieee;
2 USE ieee.std_logic_1164.ALL;
3 USE ieee.std_logic_arith.ALL;
4 USE ieee.std_logic_unsigned.ALL;
5
6 ENTITY pc IS
7 PORT(
8     clr :IN STD_LOGIC;
9     clk :IN STD_LOGIC;
10    ld :IN STD_LOGIC;
11    inc :IN STD_LOGIC;
12    d : IN STD_LOGIC_VECTOR(31 DOWNTO 0);
13    q : OUT STD_LOGIC_VECTOR(31 DOWNTO 0));
14 END pc;
15
16 ARCHITECTURE Behaviour OF pc IS
17 COMPONENT add
18 PORT (
19     A : IN STD_LOGIC_VECTOR(31 DOWNTO 0);
20     B : OUT STD_LOGIC_VECTOR(31 DOWNTO 0)
21 );
22 END COMPONENT;
23
24 COMPONENT mux2to1
25 PORT (
26     s : IN STD_LOGIC;
27     w0,w1 : IN STD_LOGIC_VECTOR(31 DOWNTO 0);
28     f : OUT STD_LOGIC_VECTOR(31 DOWNTO 0)
29 );
30 END COMPONENT;
31
32 COMPONENT register32
33 PORT(
34     d : IN STD_LOGIC_VECTOR(31 DOWNTO 0);
35     ld : IN STD_LOGIC;
36     clr: IN STD_LOGIC;
37     clk: IN STD_LOGIC;
38     Q : OUT STD_LOGIC_VECTOR(31 DOWNTO 0)
39 );
40 END COMPONENT;
41
42 SIGNAL add_out : STD_LOGIC_VECTOR(31 DOWNTO 0);
43 SIGNAL mux_out : STD_LOGIC_VECTOR(31 DOWNTO 0);
44 SIGNAL q_out : STD_LOGIC_VECTOR(31 DOWNTO 0);
45 BEGIN
46     add0: add PORT MAP(q_out, add_out);
47     mux0: mux2to1 PORT MAP(inc, d, add_out, mux_out);
48     reg0: register32 PORT MAP (mux_out, ld, clr, clk, q_out);
49     q<= q_out;
50 END Behaviour;

```

Figure 1.15: VHDL code from pc.vhd

[Figure 1.15](#) represents the VHDL code written for a program. Essentially, the program counter holds addresses of instructions, helping keep track of program execution. Executions occur incrementally. The code begins with initializing the necessary input signals including the clock, clear, load, incrementor, and data value. There is a single output representing the address, labeled as (q). By using the aforementioned add, mux2to1 and register32 components, the program counter successfully is able to execute its role. The bottom part of the code consists of the 32-bit counter (represented by 31 DOWNTO 0) to output the add, mux and q outputs. It concludes with using PORT MAP to connect the input and output signals and complete the program counter.

Data Path

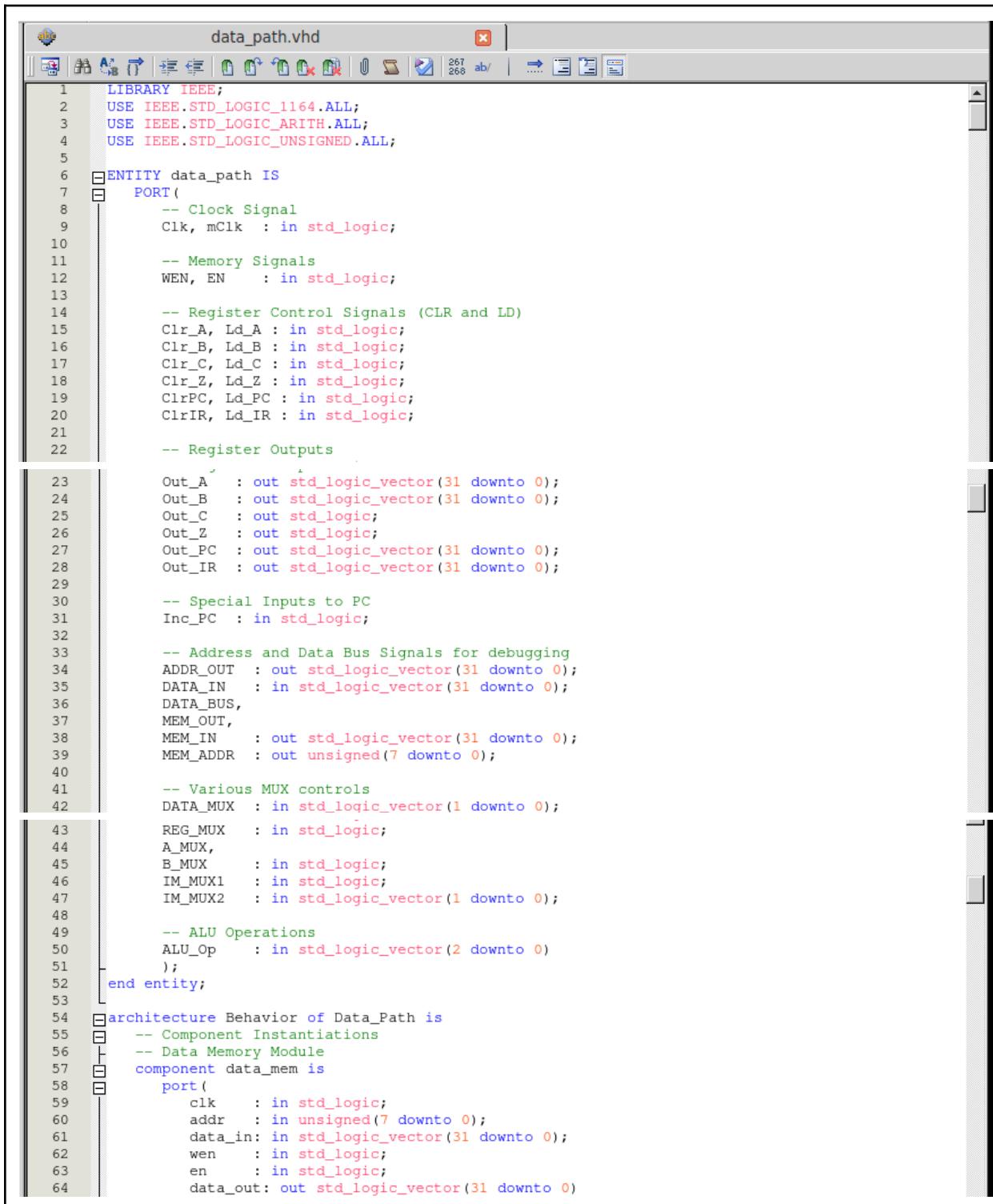

```

1 LIBRARY IEEE;
2 USE IEEE.STD_LOGIC_1164.ALL;
3 USE IEEE.STD_LOGIC_ARITH.ALL;
4 USE IEEE.STD_LOGIC_UNSIGNED.ALL;
5
6 ENTITY data_path IS
7 PORT(
8     -- Clock Signal
9     Clk, mClk : in std_logic;
10
11    -- Memory Signals
12    WEN, EN   : in std_logic;
13
14    -- Register Control Signals (CLR and LD)
15    Clr_A, Ld_A : in std_logic;
16    Clr_B, Ld_B : in std_logic;
17    Clr_C, Ld_C : in std_logic;
18    Clr_Z, Ld_Z : in std_logic;
19    ClrPC, Ld_PC : in std_logic;
20    ClrIR, Ld_IR : in std_logic;
21
22    -- Register Outputs
23    Out_A    : out std_logic_vector(31 downto 0);
24    Out_B    : out std_logic_vector(31 downto 0);
25    Out_C    : out std_logic;
26    Out_Z    : out std_logic;
27    Out_PC   : out std_logic_vector(31 downto 0);
28    Out_IR   : out std_logic_vector(31 downto 0);
29
30    -- Special Inputs to PC
31    Inc_PC   : in std_logic;
32
33    -- Address and Data Bus Signals for debugging
34    ADDR_OUT : out std_logic_vector(31 downto 0);
35    DATA_IN  : in std_logic_vector(31 downto 0);
36    DATA_BUS,
37    MEM_OUT,
38    MEM_IN   : out std_logic_vector(31 downto 0);
39    MEM_ADDR  : out unsigned(7 downto 0);
40
41    -- Various MUX controls
42    DATA_MUX  : in std_logic_vector(1 downto 0);
43    REG_MUX   : in std_logic;
44    A_MUX,
45    B_MUX    : in std_logic;
46    IM_MUX1  : in std_logic;
47    IM_MUX2  : in std_logic_vector(1 downto 0);
48
49    -- ALU Operations
50    ALU_Op   : in std_logic_vector(2 downto 0)
51 );
52 end entity;
53
54 architecture Behavior of Data_Path is
55 begin
56    -- Component Instantiations
57    -- Data Memory Module
58    component data_mem is
59        port(
60            clk      : in std_logic;
61            addr    : in unsigned(7 downto 0);
62            data_in : in std_logic_vector(31 downto 0);
63            wen     : in std_logic;
64            en      : in std_logic;
65            data_out: out std_logic_vector(31 downto 0)
66        );
67
68    end component;
69
70    data_mem1: data_mem
71        port map(
72            clk      => Clk,
73            addr    => MEM_ADDR,
74            data_in => Out_Z,
75            wen     => WEN,
76            en      => EN,
77            data_out=> Out_Z
78        );
79
80    process is
81    begin
82        wait on Inc_PC;
83        if Inc_PC = '1' then
84            PC := PC + 1;
85        end if;
86    end process;
87
88    process is
89    begin
90        wait on Out_Z;
91        if Out_Z = '1' then
92            PC := PC + 1;
93        end if;
94    end process;
95
96    process is
97    begin
98        wait on Out_Z;
99        if Out_Z = '1' then
100            PC := PC + 1;
101        end if;
102    end process;
103
104    process is
105    begin
106        wait on Out_Z;
107        if Out_Z = '1' then
988            PC := PC + 1;
989        end if;
990    end process;
991
992    process is
993    begin
994        wait on Out_Z;
995        if Out_Z = '1' then
996            PC := PC + 1;
997        end if;
998    end process;
999
1000 process is
1001 begin
1002     wait on Out_Z;
1003     if Out_Z = '1' then
1004         PC := PC + 1;
1005     end if;
1006 end process;
1007
1008 process is
1009 begin
1010     wait on Out_Z;
1011     if Out_Z = '1' then
1012         PC := PC + 1;
1013     end if;
1014 end process;
1015
1016 process is
1017 begin
1018     wait on Out_Z;
1019     if Out_Z = '1' then
1020         PC := PC + 1;
1021     end if;
1022 end process;
1023
1024 process is
1025 begin
1026     wait on Out_Z;
1027     if Out_Z = '1' then
1028         PC := PC + 1;
1029     end if;
1030 end process;
1031
1032 process is
1033 begin
1034     wait on Out_Z;
1035     if Out_Z = '1' then
1036         PC := PC + 1;
1037     end if;
1038 end process;
1039
1040 process is
1041 begin
1042     wait on Out_Z;
1043     if Out_Z = '1' then
1044         PC := PC + 1;
1045     end if;
1046 end process;
1047
1048 process is
1049 begin
1050     wait on Out_Z;
1051     if Out_Z = '1' then
1052         PC := PC + 1;
1053     end if;
1054 end process;
1055
1056 process is
1057 begin
1058     wait on Out_Z;
1059     if Out_Z = '1' then
1060         PC := PC + 1;
1061     end if;
1062 end process;
1063
1064 process is
1065 begin
1066     wait on Out_Z;
1067     if Out_Z = '1' then
1068         PC := PC + 1;
1069     end if;
1070 end process;
1071
1072 process is
1073 begin
1074     wait on Out_Z;
1075     if Out_Z = '1' then
1076         PC := PC + 1;
1077     end if;
1078 end process;
1079
1080 process is
1081 begin
1082     wait on Out_Z;
1083     if Out_Z = '1' then
1084         PC := PC + 1;
1085     end if;
1086 end process;
1087
1088 process is
1089 begin
1090     wait on Out_Z;
1091     if Out_Z = '1' then
1092         PC := PC + 1;
1093     end if;
1094 end process;
1095
1096 process is
1097 begin
1098     wait on Out_Z;
1099     if Out_Z = '1' then
1100         PC := PC + 1;
1101     end if;
1102 end process;
1103
1104 process is
1105 begin
1106     wait on Out_Z;
1107     if Out_Z = '1' then
1108         PC := PC + 1;
1109     end if;
1110 end process;
1111
1112 process is
1113 begin
1114     wait on Out_Z;
1115     if Out_Z = '1' then
1116         PC := PC + 1;
1117     end if;
1118 end process;
1119
1120 process is
1121 begin
1122     wait on Out_Z;
1123     if Out_Z = '1' then
1124         PC := PC + 1;
1125     end if;
1126 end process;
1127
1128 process is
1129 begin
1130     wait on Out_Z;
1131     if Out_Z = '1' then
1132         PC := PC + 1;
1133     end if;
1134 end process;
1135
1136 process is
1137 begin
1138     wait on Out_Z;
1139     if Out_Z = '1' then
1140         PC := PC + 1;
1141     end if;
1142 end process;
1143
1144 process is
1145 begin
1146     wait on Out_Z;
1147     if Out_Z = '1' then
1148         PC := PC + 1;
1149     end if;
1150 end process;
1151
1152 process is
1153 begin
1154     wait on Out_Z;
1155     if Out_Z = '1' then
1156         PC := PC + 1;
1157     end if;
1158 end process;
1159
1160 process is
1161 begin
1162     wait on Out_Z;
1163     if Out_Z = '1' then
1164         PC := PC + 1;
1165     end if;
1166 end process;
1167
1168 process is
1169 begin
1170     wait on Out_Z;
1171     if Out_Z = '1' then
1172         PC := PC + 1;
1173     end if;
1174 end process;
1175
1176 process is
1177 begin
1178     wait on Out_Z;
1179     if Out_Z = '1' then
1180         PC := PC + 1;
1181     end if;
1182 end process;
1183
1184 process is
1185 begin
1186     wait on Out_Z;
1187     if Out_Z = '1' then
1188         PC := PC + 1;
1189     end if;
1190 end process;
1191
1192 process is
1193 begin
1194     wait on Out_Z;
1195     if Out_Z = '1' then
1196         PC := PC + 1;
1197     end if;
1198 end process;
1199
1200 process is
1201 begin
1202     wait on Out_Z;
1203     if Out_Z = '1' then
1204         PC := PC + 1;
1205     end if;
1206 end process;
1207
1208 process is
1209 begin
1210     wait on Out_Z;
1211     if Out_Z = '1' then
1212         PC := PC + 1;
1213     end if;
1214 end process;
1215
1216 process is
1217 begin
1218     wait on Out_Z;
1219     if Out_Z = '1' then
1220         PC := PC + 1;
1221     end if;
1222 end process;
1223
1224 process is
1225 begin
1226     wait on Out_Z;
1227     if Out_Z = '1' then
1228         PC := PC + 1;
1229     end if;
1230 end process;
1231
1232 process is
1233 begin
1234     wait on Out_Z;
1235     if Out_Z = '1' then
1236         PC := PC + 1;
1237     end if;
1238 end process;
1239
1240 process is
1241 begin
1242     wait on Out_Z;
1243     if Out_Z = '1' then
1244         PC := PC + 1;
1245     end if;
1246 end process;
1247
1248 process is
1249 begin
1250     wait on Out_Z;
1251     if Out_Z = '1' then
1252         PC := PC + 1;
1253     end if;
1254 end process;
1255
1256 process is
1257 begin
1258     wait on Out_Z;
1259     if Out_Z = '1' then
1260         PC := PC + 1;
1261     end if;
1262 end process;
1263
1264 process is
1265 begin
1266     wait on Out_Z;
1267     if Out_Z = '1' then
1268         PC := PC + 1;
1269     end if;
1270 end process;
1271
1272 process is
1273 begin
1274     wait on Out_Z;
1275     if Out_Z = '1' then
1276         PC := PC + 1;
1277     end if;
1278 end process;
1279
1280 process is
1281 begin
1282     wait on Out_Z;
1283     if Out_Z = '1' then
1284         PC := PC + 1;
1285     end if;
1286 end process;
1287
1288 process is
1289 begin
1290     wait on Out_Z;
1291     if Out_Z = '1' then
1292         PC := PC + 1;
1293     end if;
1294 end process;
1295
1296 process is
1297 begin
1298     wait on Out_Z;
1299     if Out_Z = '1' then
1300         PC := PC + 1;
1301     end if;
1302 end process;
1303
1304 process is
1305 begin
1306     wait on Out_Z;
1307     if Out_Z = '1' then
1308         PC := PC + 1;
1309     end if;
1310 end process;
1311
1312 process is
1313 begin
1314     wait on Out_Z;
1315     if Out_Z = '1' then
1316         PC := PC + 1;
1317     end if;
1318 end process;
1319
1320 process is
1321 begin
1322     wait on Out_Z;
1323     if Out_Z = '1' then
1324         PC := PC + 1;
1325     end if;
1326 end process;
1327
1328 process is
1329 begin
1330     wait on Out_Z;
1331     if Out_Z = '1' then
1332         PC := PC + 1;
1333     end if;
1334 end process;
1335
1336 process is
1337 begin
1338     wait on Out_Z;
1339     if Out_Z = '1' then
1340         PC := PC + 1;
1341     end if;
1342 end process;
1343
1344 process is
1345 begin
1346     wait on Out_Z;
1347     if Out_Z = '1' then
1348         PC := PC + 1;
1349     end if;
1350 end process;
1351
1352 process is
1353 begin
1354     wait on
```

COE608: Computer Org. & Architecture > Lab 6 > The Complete CPU (Overall Project)

```
65      );
66  end component;
67
68  component register32 is
69    port(
70      d      : in std_logic_vector(31 downto 0);
71      ld     : in std_logic;
72      clr   : in std_logic;
73      clk   : in std_logic;
74      Q      : out std_logic_vector(31 downto 0)
75    );
76  end component;
77
78  -- Program Counter
79  component pc is
80    port(
81      clr : in std_logic;
82      clk : in std_logic;
83      ld  : in std_logic;
84      inc : in std_logic;
85      d   : in std_logic_vector(31 downto 0)
86      q   : out std_logic_vector(31 downto 0)
87    );
88  end component;
89
90  -- LZE
91  component LZE is
92    port( LZE_in  : in std_logic_vector(31 downto 0);
93          LZE_out : out std_logic_vector(31 downto 0)
94        );
95  end component;
96
97  -- UZE
98  component UZE is
99    port(
100    UZE_in  : in std_logic_vector(31 downto 0);
101    UZE_out : out std_logic_vector(31 downto 0)
102  );
103  end component;
104
105  -- RED
106  component RED is
107    port(
108      RED_in : in std_logic_vector(31 downto 0);
109      RED_out : out unsigned(7 downto 0)
110    );
111  end component;
112
113  -- Mux2to1
114  component mux2to1 is
115    port(
116      s      : in std_logic;
117      w0, w1 : in std_logic_vector(31 downto 0);
118      f      : out std_logic_vector(31 downto 0)
119    );
120  end component;
121
122  -- Mux4to1
123  component mux4to1 is
124    port(
125      s      : in std_logic_vector(1 downto 0);
126      X1, X2, X3, X4 : in std_logic_vector(31 downto 0);
127      f      : out std_logic_vector(31 downto 0)
```

COE608: Computer Org. & Architecture > Lab 6 > The Complete CPU (Overall Project)

```
127         f : out std_logic_vector(31 downto 0)
128     );
129 end component;
130
131 -- ALU
132 component alu is
133     port(
134         a      : in std_logic_vector(31 downto 0);
135         b      : in std_logic_vector(31 downto 0);
136         op     : in std_logic_vector(2 downto 0);
137         result : out std_logic_vector(31 downto 0);
138         zero   : out std_logic;
139         cout   : out std_logic
140     );
141 end component;
142
143 -- Signal instantiations
144 signal IR_OUT          : std_logic_vector(31 downto 0);
145 signal data_bus_s       : std_logic_vector(31 downto 0);
146 signal LZE_out_PC       : std_logic_vector(31 downto 0);
147
148 signal LZE_out_A_Mux   : std_logic_vector(31 downto 0);
149 signal LZE_out_B_Mux   : std_logic_vector(31 downto 0);
150 signal RED_out_Data_Mem : unsigned(7 downto 0);
151 signal A_Mux_out        : std_logic_vector(31 downto 0);
152 signal B_Mux_out        : std_logic_vector(31 downto 0);
153 signal reg_A_out        : std_logic_vector(31 downto 0);
154 signal reg_B_out        : std_logic_vector(31 downto 0);
155 signal reg_Mux_out      : std_logic_vector(31 downto 0);
156 signal data_mem_out    : std_logic_vector(31 downto 0);
157 signal UZB_IM_MUX1_out  : std_logic_vector(31 downto 0);
158 signal IM_MUX1_out      : std_logic_vector(31 downto 0);
159 signal LZE_IM_MUX2_out  : std_logic_vector(31 downto 0);
160 signal IM_MUX2_out      : std_logic_vector(31 downto 0);
161 signal ALU_out          : std_logic_vector(31 downto 0);
162 signal zero_flag        : std_logic;
163 signal carry_flag       : std_logic;
164 signal temp             : std_logic_vector(30 downto 0) := (others => '0');
165 signal out_pc_sig       : std_logic_vector(31 downto 0);
166
167 begin
168     IR:      register32 port map(
169         . .
170         data_bus_s,
171         Ld_IR,
172         ClrIR,
173         Clk,
174         IR_OUT
175     );
176
177     LZE_PC:   LZE port map(
178         IR_OUT,
179         LZE_out_PC
180     );
181
182     PC0:      PC port map(
183         CLR_PPC,
184         Clk,
185         ld_PPC,
186         INC_PPC,
187         LZE_out_PPC,
188         -- ADDR_OUT
189         out_Pc_sig
190     );
191
192     LZE_A_Mux: LZE port map(
193         IR_OUT,
194         LZE_out_A_Mux
195     );
196
197     A_Mux0:    mux2to1 port map(
198         A_MUX,
199         data_bus_s,
200         LZE_out_A_Mux,
201         A_Mux_out
202     );
203
204     Reg_A:     register32 port map(
205         A_Mux_out,
206         Ld_A,
207         Clr_A,
208         Clk,
209         reg_A_out
210     );
```

```
209
210  LZE_B_Mux:  LZE port map(
211    IR_OUT,
212    LZE_out_B_Mux
213  );
214
215  B_Mux0:  mux2to1 port map(
216    B_MUX,
217    data_bus_s,
218    LZE_out_B_Mux,
219    B_Mux_out
220  );
221
222  Reg_B:  register32 port map(
223    B_Mux_out,
224    Ld_B,
225    Clr_B,
226    Clk,
227    reg_B_out
228  );
229
230  Reg_Mux0:  mux2to1 port map(
231    REG_MUX,
232    Reg_A_out,
233    Reg_B_out,
234    Reg_Mux_out
235  );
236
237  RED_Data_Mem: RED port map(
238    IR_OUT,
239    RED_out_data_mem
240  );
241
242  Data_Mem0:  data_mem port map(
243    mClk,
244    RED_out_data_mem,
245    Reg_Mux_out,
246    WEN,
247    EN,
248    data_mem_out
249  );
250
251  UZE_IM_MUX1: UZE port map(
252    IR_OUT,
253    UZE_IM_MUX1_out
254  );
255
256  IM_MUX1a:  mux2to1 port map(
257    IM_MUX1,
258    reg_A_out,
259    UZE_IM_MUX1_out,
260    IM_MUX1_out
261  );
262
263  LZE_IM_MUX2: LZE port map(
264    IR_OUT,
265    LZE_IM_MUX2_out
266  );
267
268  IM_MUX2a:  mux4to1 port map(
269    IM_MUX2,
270    reg_B_out,
271    LZE_IM_MUX2_out,
```

```

272      (temp &'1'),
273      (others => '0'),
274      IM_MUX2_out
275      );
276
277  ALU0:      ALU port map(
278    IM_MUX1_out,
279    IM_MUX2_out,
280    ALU_OP,
281    ALU_out,
282    zero_flag ,
283    carry_flag
284  );
285
286  DATA_MUX0: mux4tol port map(
287    DATA_MUX,
288    DATA_IN,
289    data_mem_out,
290    ALU_out,
291    (others => '0'),
292    data_bus_s
293  );
294
295  DATA_BUS <= data_bus_s;
296  OUT_A <= reg_A_out;
297  OUT_B <= reg_B_out;
298  OUT_IR <= IR_OUT;
299  ADDR_OUT <= out_pc_sig;
300  OUT_PC <= out_pc_sig;
301
302  MEM_ADDR <= RED_out_Data_Mem;
303  MEM_IN <= Reg_Mux_out;
304  MEM_OUT <= data_mem_out;
305
306 end Behavior;

```

Figure 1.16: VHDL code from data_path.vhd

Figure 1.16 Represents all of the aforementioned scripts. It begins with initializing the clock signal, memory signals and register control signals, all inputs for the system. Register Output A follows, with inputs to the PC, Address, Mux controls and ALU operations. Past this, The different parts of the architecture are implemented. This includes the Data Memory module, PC, LZE, UZE, RED, Mux 2-to-1, Mux 4-to-1, and ALU. Signals are installed, and PORT MAP is used to connect and implement all of the signals and calculations, resulting in us getting the final required results.

Control Unit

Quartus II 32-bit - /home/student1/r225shar/Desktop/COE608/lab5/lab5 - lab5

File Edit View Insert Tools Window Help

control.vhd

```
library ieee;
use ieee.std_logic_1164.all;

entity control is
  port(
    cik, mclk : IN STD_LOGIC;
    enable : IN STD_LOGIC;
    status, status1 : IN STD_LOGIC;
    en : IN STD_LOGIC;
    A_Mux, B_Mux : OUT STD_LOGIC;
    IM_MUX1, REG_Mux : OUT STD_LOGIC;
    ALU_op : OUT STD_LOGIC_VECTOR(2 DOWNTO 0);
    inc_FC, id_FC : OUT STD_LOGIC;
    inc_Z, id_Z : OUT STD_LOGIC;
    id_IR : OUT STD_LOGIC;
    cir_A, cir_B, cir_C, cir_Z : OUT STD_LOGIC;
    B_MUX : OUT STD_LOGIC;
    T : OUT STD_LOGIC_VECTOR(5 DOWNTO 0);
    wen, en : OUT STD_LOGIC
  );
end control;

ARCHITECTURE description of control IS
  TYPE STATETYPE IS (state_0, state_1, state_2);
  SIGNAL present_state: STATETYPE;
  SIGNAL Instruction_sig: STD_LOGIC_VECTOR(3 DOWNTO 0);
  SIGNAL Instruction_sig2: STD_LOGIC_VECTOR(7 DOWNTO 0);
BEGIN
  Instruction_sig<= INST(31 DOWNTO 28);
  Instruction_sig2<= INST(31 DOWNTO 24);

  ---- OPERATION DECODER ----
  PROCESS(present_state, inst, status, status1, enable, Instruction_sig, Instruction_sig2)
  BEGIN
    if enable = '1' then
      if present_state = state_0 then
        DATA_Mux <= "000"; -- Fetch Address of Next Instruction
        cir_IR <= '0';
        id_IR <= '0';
        inc_FC <= '0';
        cir_A <= '0';
        id_A <= '0';
        id_B <= '0';
        cir_B <= '0';
        cir_C <= '0';
        id_C <= '0';
        id_Z <= '0';
        cir_Z <= '0';
        id_Z <= '0';
        en <= '0';
        wen <= '0';

        cir_Z <= '0';
        id_Z <= '0';
        wen <= '0';

        cir_IR <= '0'; -- INCREMENT PC COUNTER
        id_IR <= '0';
        id_FC <= '1';
        inc_FC <= '1';
        cir_A <= '0';
        id_A <= '0';
        id_B <= '0';
        cir_B <= '0';
        cir_C <= '0';
        id_C <= '0';
        id_Z <= '0';
        cir_Z <= '0';
        id_Z <= '0';
        en <= '1';
        wen <= '1';

        if Instruction.sig = "0010" then -- STA
          cir_IR <= '0';
          id_IR <= '0';
          id_FC <= '1';
          inc_FC <= '1';
          cir_A <= '0';
          id_A <= '0';
          id_B <= '0';
          cir_B <= '0';
          cir_C <= '0';
          id_C <= '0';

          cir_Z <= '0';
          id_Z <= '0';
          wen <= '1';

          REG_Mux <= '1';
          DATA_Mux <= "000";
          en <= '1';
          wen <= '1';

        elsif Instruction.sig = "0011" then -- STB
          cir_IR <= '0';
          id_IR <= '0';
          id_FC <= '1';
          inc_FC <= '1';
          cir_A <= '0';
          id_A <= '0';
          id_B <= '0';
          cir_B <= '0';
          cir_C <= '0';
          id_C <= '0';

          cir_Z <= '0';
          id_Z <= '0';
          wen <= '1';

          en <= '1';
          wen <= '1';

        elsif Instruction.sig = "0101" then -- LDA
          cir_IR <= '0';
          id_IR <= '0';
          id_FC <= '1';
          inc_FC <= '1';
          cir_A <= '0';
          id_A <= '0';
          id_B <= '0';
          cir_B <= '0';
          cir_C <= '0';
          id_C <= '0';

          cir_Z <= '0';
          id_Z <= '0';
          B_MUX <= '0';
          DATA_Mux <= "001";
          en <= '1';
          wen <= '0';

        end if; -- END IF FOR LOAD STORE IN STAGE 1

        elsif present_state = state_2 then
          if Instruction.sig = "0101" then -- JUMP
            cir_IR <= '0';

          end if;
        end if;
      end if;
    end process;
  end if;
end control;
```

COE608: Computer Org. & Architecture > Lab 6 > The Complete CPU (Overall Project)

```

146      id_IR <= '0';
147      id_PC <= '1';
148      id_FC <= '1';
149      cir_IR <= '0';
150      id_A <= '0';
151      id_B <= '0';
152      cir_B <= '0';
153      cir_C <= '0';
154      id_C <= '0';
155      cir_Z <= '0';
156      id_Z <= '0';
157
158      elsif instruction_sig = "0110" then -- BEQ
159          cir_IR <= '0';
160          id_A <= '1';
161          id_PC <= '1';
162          inc_FC <= '0';
163          cir_A <= '1';
164          id_A <= '0';
165          id_B <= '0';
166          cir_B <= '0';
167          id_C <= '0';
168          cir_C <= '0';
169          id_Z <= '0';
170          id_Z <= '0';
171
172      elsif instruction_sig = "1000" then -- BNE
173          cir_IR <= '0';
174          id_A <= '0';
175          id_B <= '1';
176          id_FC <= '1';
177          cir_A <= '0';
178          id_A <= '1';
179          id_B <= '0';
180          cir_B <= '0';
181          cir_C <= '0';
182          id_C <= '0';
183          cir_Z <= '0';
184          id_Z <= '0';
185
186      elsif instruction_sig = "1001" then -- LDA
187          cir_IR <= '0';
188          id_A <= '0';
189          id_FC <= '0';
190          inc_FC <= '0';
191          cir_A <= '1';
192          id_A <= '1';
193          id_B <= '0';
194          cir_B <= '0';
195          id_C <= '0';
196          id_D <= '0';
197          id_E <= '0';
198          id_F <= '0';
199          id_Mux <= '0';
200          DATA_MUX <= "011";
201          en <= '1';
202          wen <= '0';
203
204      elsif instruction_sig = "1010" then -- LDH
205          cir_IR <= '0';
206          id_A <= '0';
207          id_B <= '1';
208          inc_FC <= '0';
209          cir_A <= '0';
210          id_A <= '1';
211          id_B <= '0';
212          cir_B <= '0';
213          id_C <= '0';
214          id_D <= '0';
215          cir_Z <= '0';
216          id_Z <= '0';
217          B_Mux <= '0';
218          DATA_MUX <= "01";
219          en <= '1';
220          wen <= '0';
221
222      elsif instruction_sig = "0010" then -- STA
223          cir_IR <= '0';
224          id_A <= '0';
225          id_B <= '1';
226          inc_FC <= '0';
227          cir_A <= '0';
228          id_A <= '1';
229          id_B <= '0';
230          cir_B <= '0';
231          id_C <= '0';
232          id_D <= '0';
233          id_E <= '0';
234          id_F <= '0';
235          REG_Mux <= '0';
236          DATA_MUX <= "000";
237          en <= '1';
238          wen <= '1';
239
240      elsif instruction_sig = "0011" then -- STB
241          cir_IR <= '0';
242
243          id_IR <= '0';
244          id_FC <= '0';
245          inc_FC <= '0';
246          cir_A <= '0';
247          id_A <= '0';
248          id_B <= '0';
249          cir_B <= '0';
250          id_C <= '0';
251          id_D <= '0';
252          id_E <= '0';
253          REG_Mux <= '1';
254          DATA_MUX <= "000";
255          en <= '1';
256          wen <= '1';
257
258      elsif instruction_sig = "0000" then -- LDAI
259          cir_IR <= '0';
260          id_A <= '0';
261          id_FC <= '0';
262          inc_FC <= '0';
263          cir_A <= '0';
264          id_A <= '1';
265          id_B <= '0';
266          cir_B <= '0';
267          id_C <= '0';
268          id_D <= '0';
269          cir_Z <= '0';
270          id_E <= '0';
271          A_Mux <= '1';
272
273      elsif instruction_sig = "0001" then -- LDHI
274          cir_IR <= '0';
275          id_A <= '0';
276          id_B <= '1';
277          inc_FC <= '0';
278          cir_A <= '0';
279          id_A <= '1';
280          id_B <= '0';
281          cir_B <= '0';
282          id_C <= '0';
283          id_D <= '0';
284          cir_Z <= '0';
285          id_E <= '0';
286          B_Mux <= '1';
287
288      elsif instruction_sig = "0100" then -- LUI
289          cir_IR <= '0';

```

COE608: Computer Org. & Architecture > Lab 6 > The Complete CPU (Overall Project)

```

280      id_IR <= '0';
281      id_PC <= '0';
282      inc_PC <= '0';
283      cir_A <= '0';
284      cir_B <= '0';
285      id_B <= '0';
286      cir_B <= '1';
287      cir_C <= '0';
288      id_C <= '0';
289      cir_Z <= '0';
290      id_Z <= '0';
291      ALU_op <= "001";
292      A_MUX <= '0';
293      DATA_MUX <= "000";
294      im_MUX1 <= '0';
295      im_MUX2 <= '0';
296
297      elsif Instruction_sig2 = "01111001" then -- ANDI
298
299          cir_IR <= '0';
300          id_IR <= '0';
301          id_PC <= '0';
302          inc_PC <= '0';
303          cir_A <= '0';
304          id_A <= '1';
305          cir_B <= '0';
306          cir_B <= '0';
307          cir_C <= '0';
308          id_B <= '1';
309          cir_Z <= '0';
310          id_Z <= '1';
311          cir_A <= '0';
312          id_A <= '1';
313          cir_B <= '0';
314          cir_B <= '0';
315          cir_C <= '0';
316          id_B <= '1';
317          cir_Z <= '0';
318          id_Z <= '1';
319          ALU_op <= "0000";
320          A_MUX <= '0';
321          DATA_MUX <= "10";
322          im_MUX1 <= '1';
323          im_MUX2 <= '01';
324
325
326      elsif Instruction_sig2 = "01111110" then -- DECA
327
328          cir_IR <= '0';
329          id_IR <= '0';
330          inc_PC <= '0';
331          cir_A <= '0';
332          id_A <= '0';
333          cir_B <= '0';
334          cir_C <= '0';
335          id_B <= '0';
336          cir_Z <= '0';
337          id_Z <= '1';
338
339          ALU_op <= "110";
340          A_MUX <= '0';
341          DATA_MUX <= "10";
342          im_MUX1 <= '0';
343          im_MUX2 <= '10';
344
345
346      elsif Instruction_sig2 = "01111000" then -- ADD
347
348          cir_IR <= '0';
349          id_IR <= '0';
350          id_PC <= '0';
351          inc_PC <= '0';
352          cir_A <= '0';
353          id_A <= '1';
354          cir_B <= '0';
355          cir_C <= '0';
356          id_B <= '0';
357          cir_Z <= '0';
358          id_Z <= '1';
359          ALU_op <= "110";
360          A_MUX <= '0';
361          DATA_MUX <= "10";
362          im_MUX1 <= '0';
363          im_MUX2 <= '10';
364
365
366      elsif Instruction.sig2 = "01110010" then -- SUB
367
368          cir_IR <= '0';
369          id_IR <= '0';
370          id_PC <= '0';
371          inc_PC <= '0';
372          cir_A <= '0';
373          id_A <= '1';
374          cir_B <= '0';
375          cir_C <= '0';
376          id_B <= '1';
377          cir_Z <= '0';
378          id_Z <= '1';
379          ALU_op <= "110";
380          A_MUX <= '0';
381          DATA_MUX <= "10";
382          im_MUX1 <= '0';
383          im_MUX2 <= '00';
384
385
386      elsif Instruction.sig2 = "01110011" then -- INCA
387
388          cir_IR <= '0';
389          id_IR <= '0';
390          id_PC <= '0';
391          inc_PC <= '0';
392          cir_A <= '0';
393          id_A <= '1';
394          cir_B <= '0';
395          cir_C <= '0';
396          id_B <= '0';
397          cir_Z <= '0';
398          id_Z <= '1';
399          im_MUX1 <= '0';
400
401          ALU_op <= "010";
402          A_MUX <= '0';
403          DATA_MUX <= "00";
404          im_MUX2 <= '0';
405
406
407      elsif Instruction.sig2 = "01111011" then -- AND
408
409          cir_IR <= '0';
410          id_IR <= '0';
411          id_PC <= '0';
412          inc_PC <= '0';
413          cir_A <= '0';
414          id_A <= '1';
415          cir_B <= '0';
416          cir_C <= '0';
417          id_B <= '0';
418          cir_Z <= '0';
419          id_Z <= '1';
420
421          ALU_op <= "000";
422          A_MUX <= '0';
423          DATA_MUX <= "00";
424          im_MUX1 <= '0';
425          im_MUX2 <= '00';
426
427
428      elsif Instruction.sig2 = "01110001" then -- ADDI
429
430          cir_IR <= '0';
431          id_IR <= '0';
432          id_PC <= '0';
433          inc_PC <= '0';
434          cir_A <= '0';
435          id_A <= '1';
436          cir_B <= '0';
437          cir_C <= '0';
438          id_B <= '0';
439          cir_Z <= '0';
440          id_Z <= '1';
441          cir_A <= '0';
442          id_A <= '1';
443          cir_B <= '0';
444          cir_C <= '0';
445          id_B <= '0';
446          cir_Z <= '0';
447          id_Z <= '1';
448          ALU_op <= "010";
449
450
451

```

COE608: Computer Org. & Architecture > Lab 6 > The Complete CPU (Overall Project)

```

436      ... ...
437      A_Mux <= '0';
438      DATA_Mux <= "10";
439      id_A <= '0';
440      in_MUX2 <= "01";
441
442      elsif Instruction_sig2 = "01111101" then -- ORI
443          clr_IR <= '0';
444          id_IR <= '0';
445          id_A <= '1';
446          inc_PC <= '0';
447          clr_A <= '0';
448          id_A <= '0';
449          id_B <= '0';
450          clr_B <= '0';
451          id_B <= '1';
452          inc_PC <= '1';
453          A_Mux <= '01';
454          DATA_Mux <= "10";
455          id_C <= '0';
456          in_MUX2 <= "01";
457
458      elsif Instruction_sig2 = "01110100" then -- ROL
459          clr_IR <= '0';
460          id_IR <= '0';
461          id_A <= '1';
462          inc_PC <= '0';
463          clr_A <= '0';
464          id_A <= '1';
465          id_B <= '0';
466          clr_B <= '0';
467          id_B <= '1';
468          id_C <= '1';
469          clr_Z <= '0';
470          id_C <= '0';
471          A_Mux <= "100";
472          DATA_Mux <= '01';
473          id_MUX1 <= '0';
474          id_MUX2 <= '0';
475
476      elsif Instruction_sig2 = "01111111" then -- ROR
477          clr_IR <= '0';
478          id_IR <= '0';
479          id_A <= '1';
480          inc_PC <= '0';
481          clr_A <= '0';
482
483          ... ...
484          id_B <= '0';
485          clr_B <= '0';
486          id_C <= '0';
487          id_C <= '1';
488          clr_Z <= '0';
489          id_Z <= '1';
490          A_Mux <= "101";
491          DATA_Mux <= "10";
492          id_MUX1 <= '1';
493          id_MUX2 <= '0';
494
495      elsif Instruction_sig2 = "01110101" then -- CLR_A
496          clr_IR <= '0';
497          id_IR <= '0';
498          id_FC <= '0';
499          id_A <= '1';
500          clr_A <= '1';
501          id_A <= '0';
502          id_B <= '0';
503          clr_B <= '0';
504          id_B <= '1';
505          id_Z <= '0';
506          id_Z <= '0';
507
508      elsif Instruction_sig2 = "01110110" then -- CLR_B
509          clr_IR <= '0';
510          id_IR <= '0';
511          id_FC <= '0';
512          inc_PC <= '0';
513          clr_A <= '0';
514          id_A <= '0';
515          id_B <= '0';
516          clr_B <= '1';
517          id_B <= '0';
518          id_C <= '0';
519          id_C <= '0';
520          id_Z <= '0';
521
522      elsif Instruction_sig2 = "01110111" then -- CLR_C
523          clr_IR <= '0';
524          id_IR <= '0';
525          id_FC <= '0';
526          id_A <= '0';
527          clr_A <= '0';
528          id_A <= '0';
529          id_B <= '0';
530
531          ... ...
532          id_B <= '0';
533          id_C <= '0';
534          id_D <= '0';
535
536      elsif Instruction_sig2 = "01110111" then -- CLR_Z
537          clr_IR <= '0';
538          id_IR <= '0';
539          id_FC <= '0';
540          inc_PC <= '0';
541          id_A <= '0';
542          id_A <= '1';
543          id_B <= '0';
544          id_B <= '0';
545          id_C <= '0';
546          id_C <= '1';
547          id_D <= '0';
548          id_D <= '1';
549          id_Z <= '0';
550
551      elsif Instruction_sig2 = "01111010" then -- TSTZ
552          if (status < '1') then
553              clr_IR <= '0'; -- INCREMENT PC COUNTER
554              id_IR <= '0';
555              id_FC <= '0';
556              inc_PC <= '1';
557              clr_A <= '0';
558              id_A <= '0';
559              id_B <= '0';
560              id_B <= '1';
561              id_C <= '0';
562              id_C <= '1';
563              id_D <= '0';
564              id_D <= '0';
565          end if;
566
567      elsif Instruction_sig2 = "01111100" then -- TSTC
568          if (status < '1') then
569              clr_IR <= '0'; -- INCREMENT PC COUNTER
570              id_IR <= '0';
571              id_FC <= '0';
572              inc_PC <= '1';
573              clr_A <= '0';
574              id_A <= '0';
575              id_B <= '0';
576              id_C <= '0';
577              id_C <= '1';

```

```

578      clr_Z <= '0';
579      ld_Z <= '0';
580    end if;
581  end if; -- For state 2 Ops
582  end if; -- For Enable
583 END process;
584
585 ----- STATE MACHINE -----
586 PROCESS (clk, enable)
587 begin
588   if enable = '1' then
589     if rising_edge (clk) then
590       if present_state = state_0 then present_state <= state_1;
591     elsif present_state = state_1 then present_state <= state_2;
592     else present_state <= state_0;
593   end if;
594   end if;
595   else present_state <= state_0;
596   end if;
597 END process;
598
599
600 WITH present_state select
601   T <= "001" when state_0,
602   "010" when state_1,
603   "100" when state_2,
604   "001" when others;
605 END description;
606

```

Figure 1.17: VHDL code from control.vhd

The Control.vhd file in [Figure 1.17](#) represents the main functionality of the system for the control unit design. Following Lab 4B, the control VHDL file combines the functionality of a state generator, memory signal generator and decoder with the various inputs to create various outputs. The state generator makes use of the enable (en) and clock (clk) to produce the state, which is used in the decoder. The memory signal generator makes use of the clock (clk), memory clock (mclk) and instruction (INST) inputs, to produce outputs wen (write enable) and enable (en). Finally the decoder block makes use of the inputs instruction (inst), status carry (status_c) and status zero (status_z) to produce the various outputs from lab 4b such as load instruction register (LD_IR), clear instruction register (CLR_IR), load register a (LDA), clear register a (CLR_A), ..., Multiplexers 1 and 2 and Register Multiplexer (Reg_MUX).

Control Processor Unit 1

```
LIBRARY ieee;
USE ieee.std_logic_1164.all;
USE ieee.std_logic_arith.all;
USE ieee.std_logic_unsigned.all;

ENTITY cpul IS
PORT (
clk : IN STD_LOGIC;
mem_clk : IN STD_LOGIC;
rst : IN STD_LOGIC;
dataIn : IN STD_LOGIC_VECTOR(31 DOWNTO 0);
dataOut : OUT STD_LOGIC_VECTOR(31 DOWNTO 0);
addrOut : OUT STD_LOGIC_VECTOR(31 DOWNTO 0);
dOutA : OUT STD_LOGIC_VECTOR(31 DOWNTO 0);
dOutB : OUT STD_LOGIC_VECTOR(31 DOWNTO 0);
doutC : OUT STD_LOGIC;
doutZ : OUT STD_LOGIC;
dOutIR : OUT STD_LOGIC_VECTOR(31 DOWNTO 0);
dOutPC : OUT STD_LOGIC_VECTOR(31 DOWNTO 0);
wEn : OUT STD_LOGIC;
outT : OUT STD_LOGIC_VECTOR(2 DOWNTO 0);
wen_mem : OUT STD_LOGIC;
en_mem : OUT STD_LOGIC
);
END cpul;

ARCHITECTURE description OF cpul IS
COMPONENT Data_Path IS
PORT (
Clk, mClk : IN STD_LOGIC; -- clock Signal
--Memory Signals
WEN, EN : IN STD_LOGIC;
-- Register Control Signals (CLR and LD).
Clr_A , Ld_A : IN STD_LOGIC;
Clr_B , Ld_B : IN STD_LOGIC;
Clr_C , Ld_C : IN STD_LOGIC;
Clr_Z , Ld_Z : IN STD_LOGIC;
ClrPC , Ld_PC : IN STD_LOGIC;
ClrIR , Ld_IR : IN STD_LOGIC;
```

```

Out_A : OUT STD_LOGIC_VECTOR(31 DOWNTO 0);
Out_B : OUT STD_LOGIC_VECTOR(31 DOWNTO 0);
Out_C : OUT STD_LOGIC;
Out_Z : OUT STD_LOGIC;
Out_PC : OUT STD_LOGIC_VECTOR(31 DOWNTO 0);
Out_IR : OUT STD_LOGIC_VECTOR(31 DOWNTO 0);
-- Special inputs to PC.
Inc_PC : IN STD_LOGIC;
-- Address and Data Bus signals for debugging.
ADDR_OUT : OUT STD_LOGIC_VECTOR(31 DOWNTO 0);
DATA_IN : IN STD_LOGIC_VECTOR(31 DOWNTO 0);
DATA_BUS, MEM_OUT, MEM_IN : OUT STD_LOGIC_VECTOR(31 DOWNTO 0);
MEM_ADDR : OUT STD_LOGIC_VECTOR(7 DOWNTO 0);
-- Various MUX controls.
DATA_Mux : IN STD_LOGIC_VECTOR(1 DOWNTO 0);
REG_Mux : IN STD_LOGIC;
A_MUX, B_MUX : IN STD_LOGIC;
IM_MUX1 : IN STD_LOGIC;
IM_MUX2 : IN STD_LOGIC_VECTOR(1 DOWNTO 0);
-- ALU Operations.
ALU_Op : IN STD_LOGIC_VECTOR(2 DOWNTO 0)
);
END COMPONENT;

COMPONENT Control_NEW IS
PORT (
clk, mclk : IN STD_LOGIC;
enable : IN STD_LOGIC;
statusC, statusZ : IN STD_LOGIC;
INST : IN STD_LOGIC_VECTOR(31 DOWNTO 0);
A_Mux, B_Mux : OUT STD_LOGIC;
IM_MUX1, REG_Mux : OUT STD_LOGIC;
IM_MUX2, DATA_Mux : OUT STD_LOGIC_VECTOR(1 DOWNTO 0);
ALU_op : OUT STD_LOGIC_VECTOR(2 DOWNTO 0);
inc_PC, ld_PC : OUT STD_LOGIC;
clr_IR : OUT STD_LOGIC;
ld_IR : OUT STD_LOGIC;
clr_A, clr_B, clr_C, clr_Z : OUT STD_LOGIC;
ld_A, ld_B, ld_C, ld_Z : OUT STD_LOGIC;

```

```

ld_A, ld_B, ld_C, ld_Z : OUT STD_LOGIC;
T : OUT STD_LOGIC_VECTOR(2 DOWNTO 0);
wen, en : OUT STD_LOGIC
);
END COMPONENT;

COMPONENT reset_circuit IS
PORT (
Reset : IN STD_LOGIC;
Clk : IN STD_LOGIC;
Enable_PD : OUT STD_LOGIC;
Clr_PC : OUT STD_LOGIC
);
END COMPONENT;

SIGNAL dp_mux1, dp_clrA, dp_ldA, dp_clrB, dp_ldB, dp_clrC, dp_ldC, dp_clrZ,
dp_ldZ, memWEN, memEN, dp_muxA, dp_muxB : STD_LOGIC;
SIGNAL mux_data, reg, enpd, irlc, pinc, pclr, pcld, out0, out1, out7, out6 : STD_LOGIC;
SIGNAL outIR : STD_LOGIC_VECTOR(31 DOWNTO 0);
SIGNAL alu : STD_LOGIC_VECTOR(2 DOWNTO 0);
SIGNAL dp_mux2, dp_muxData : STD_LOGIC_VECTOR(1 DOWNTO 0);

BEGIN
dat : Data_Path
PORT MAP(
Clk => clk,
mClk => mem_clk,
WEN => memWEN,
EN => memEN,
Clr_A => dp_clrA,
Ld_A => dp_ldA, Clr_B => dp_clrB, Ld_B => dp_ldB, Clr_C => dp_clrC, Ld_C
=> dp_ldC, Clr_Z => dp_clrZ, Ld_Z => dp_ldZ,
ClrPC => pclr, Ld_PC => pcld, ClrIR => irlc, Ld_IR => irld,
Out_A => dOutA, Out_B => dOutB, Out_C => out0, Out_Z => out1, Out_PC =>
dOutPC, Out_IR => outIR, Inc_PC => pinc,
ADDR_OUT => addrOut, DATA_IN => dataIn, DATA_BUS => dataOut, DATA_Mux
=> dp_muxData, REG_Mux => reg, A_MUX => dp_muxA, B_MUX => dp_muxB, IM_MUX1 =>
dp_mux1, IM_MUX2 => dp_mux2,
ALU_Op => alu
);

control_unit : Control_NEW
PORT MAP(
clk => clk, mclk => mem_clk, enable => enpd, statusC => out0, statusZ =>
out1, INST => outIR,
A_Mux => dp_muxA, B_Mux => dp_muxB, IM_MUX1 => dp_mux1, REG_Mux => reg,
IM_MUX2 => dp_mux2, DATA_Mux => dp_muxData,
ALU_op => alu, inc_PC => pinc, ld_PC => pcld, clr_IR => irlc, ld_IR =>
irld,
clr_A => dp_clrA, clr_B => dp_clrB, clr_C => dp_clrC, clr_Z => dp_clrZ,
ld_A => dp_ldA, ld_B => dp_ldB, ld_C => dp_ldC, ld_Z => dp_ldZ,
T => outT, wen => memWEN, en => memEN
);

reset : reset_circuit
PORT MAP(
Reset => rst,
Clk => clk,
Enable_PD => enpd,
Clr_PC => pclr
);
dOutC <= out0;
dOutZ <= out1;
dOutIR <= outIR;
wen_mem <= out7;
en_mem <= out6;
END description;

```

Figure 1.18: VHDL code from cpul.vhd

Figure 1.18 represents the CPU1.vhd file, which assigns and puts together the architecture of the PC. It consists of the different mux controls, ALU operations, inputs for the PC and the necessary outputs.

CPU Test Simulation

```

library ieee;
use ieee.std_logic_1164.all;

ENTITY CPU_TEST_Sim IS
PORT(
    cpuClk : in std_logic;
    memClk : in std_logic;
    rst : in std_logic;
    -- Debug data.
    outA, outB : out std_logic_vector(31 downto 0);
    outC, outZ : out std_logic;
    outIR : out std_logic_vector(31 downto 0);
    outPC : out std_logic_vector(31 downto 0);
    -- Processor-Inst Memory Interface.
    addrOut : out std_logic_vector(5 downto 0);
    wEn : out std_logic;
    memDataOut : out std_logic_vector(31 downto 0);
    memDataIn : out std_logic_vector(31 downto 0);
    -- Processor State
    T_Info : out std_logic_vector(2 downto 0);
    --data Memory Interface
    wen_mem, en_mem : out std_logic);
END CPU_TEST_Sim;

ARCHITECTURE behavior OF CPU_TEST_Sim IS
COMPONENT system_memory
PORT(
    address : IN STD_LOGIC_VECTOR (5 DOWNTO 0);
    clock : IN STD_LOGIC ;
    data : IN STD_LOGIC_VECTOR (31 DOWNTO 0);
    wren : IN STD_LOGIC ;
    q : OUT STD_LOGIC_VECTOR (31 DOWNTO 0)
);
END COMPONENT;
COMPONENT cpul
PORT(
    clk : in std_logic;
    mem_clk : in std_logic;
    rst : in std_logic;
    dataIn : in std_logic_vector(31 downto 0);
    dataOut : out std_logic_vector(31 downto 0);
    addrOut : out std_logic_vector(31 downto 0);
    wEn : out std_logic;
    doutA, doutB : out std_logic_vector(31 downto 0);
    doutC, doutZ : out std_logic;
    doutIR : out std_logic_vector(31 downto 0);
    doutPC : out std_logic_vector(31 downto 0);
    outT : out std_logic_vector(2 downto 0);
    wen_mem, en_mem : out std_logic);
END COMPONENT;
BEGIN
-- Component instantiations.
main_memory : system_memory
PORT MAP(
    address => add_from_cpu(5 downto 0),
    clock => memClk,
    data => cpu_to_mem,
    wren => wen_from_cpu,
    q => mem_to_cpu
);
main_processor : cpul
PORT MAP(
    clk => cpuClk,
    mem_clk => memClk,
    rst => rst,
    dataIn => mem_to_cpu,
    dataOut => cpu_to_mem,
    addrOut => add_from_cpu,
    wEn => wen_from_cpu,
    doutA => outA,
    doutB => outB,
    doutC => outC,
    doutZ => outZ,
    dOutIR => outIR,
    dOutPC => outPC,
    outT => T_Info,
    wen_mem => wen_mem,
    en_mem => en_mem
);
addrOut <= add_from_cpu(5 downto 0);
wEn <= wen_from_cpu;
memDataOut <= mem_to_cpu;
memDataIn <= cpu_to_mem;
END behavior;

```

Figure 1.19: VHDL code from cpu_test_sim.vhd

Figure 1.19 represents the code for the control processor unit testing simulation, which is in VHDL.

System Memory

```

LIBRARY ieee;
USE ieee.std_logic_1164.all;

LIBRARY altera_mf;
USE altera_mf.all;

ENTITY system_memory IS
  PORT
  (
    address      : IN STD_LOGIC_VECTOR (5 DOWNTO 0);
    clock        : IN STD_LOGIC := '1';
    data         : IN STD_LOGIC_VECTOR (31 DOWNTO 0);
    wren         : IN STD_LOGIC ;
    q            : OUT STD_LOGIC_VECTOR (31 DOWNTO 0)
  );
END system_memory;

ARCHITECTURE SYN OF system_memory IS
  SIGNAL sub_wire0 : STD_LOGIC_VECTOR (31 DOWNTO 0);

  COMPONENT altsyncram
  GENERIC (
    clock_enable_input_a      : STRING;
    clock_enable_output_a     : STRING;
    init_file                : STRING;
    intended_device_family   : STRING;
    lpm_hint                 : STRING;
    lpm_type                 : STRING;
    numwords_a               : NATURAL;
    operation_mode           : STRING;
    outdata_aclr_a           : STRING;
    outdata_reg_a             : STRING;
    power_up_uninitialized   : STRING;
    widthad_a                : NATURAL;
    width_a                  : NATURAL;
    width_byteena_a          : NATURAL
  );
  PORT (
    address_a    : IN STD_LOGIC_VECTOR (5 DOWNTO 0);
    clock0       : IN STD_LOGIC ;
    data_a       : IN STD_LOGIC_VECTOR (31 DOWNTO 0);
    wren_a       : IN STD_LOGIC ;
    q_a          : OUT STD_LOGIC_VECTOR (31 DOWNTO 0)
  );
  END COMPONENT;
BEGIN
  q    <= sub_wire0(31 DOWNTO 0);

  altsyncram_component : altsyncram
  GENERIC MAP (
    clock_enable_input_a => "BYPASS",
    clock_enable_output_a => "BYPASS",
    init_file => "system_memory.mif",
    intended_device_family => "Cyclone II",
    lpm_hint => "ENABLE_RUNTIME_MOD=NO",
    lpm_type => "altsyncram",
    numwords_a => 64,
    operation_mode => "SINGLE_PORT",
    outdata_aclr_a => "NONE",
    outdata_reg_a => "CLOCK0",
    power_up_uninitialized => "FALSE",
    widthad_a => 6,
    width_a => 32,
    width_byteena_a => 1
  )
  PORT MAP (
    address_a => address,
    clock0 => clock,
    data_a => data,
    wren_a => wren,
    q_a => sub_wire0
  );
END SYN;

```

Figure 1.20: VHDL code from system_memory.vhd

Figure 1.20 represents the code for the system memory. In order to represent memory for different parts of the CPU, the memory file values can be altered.

Part II - The Complete CPU System

CPU Test Simulation Waveform

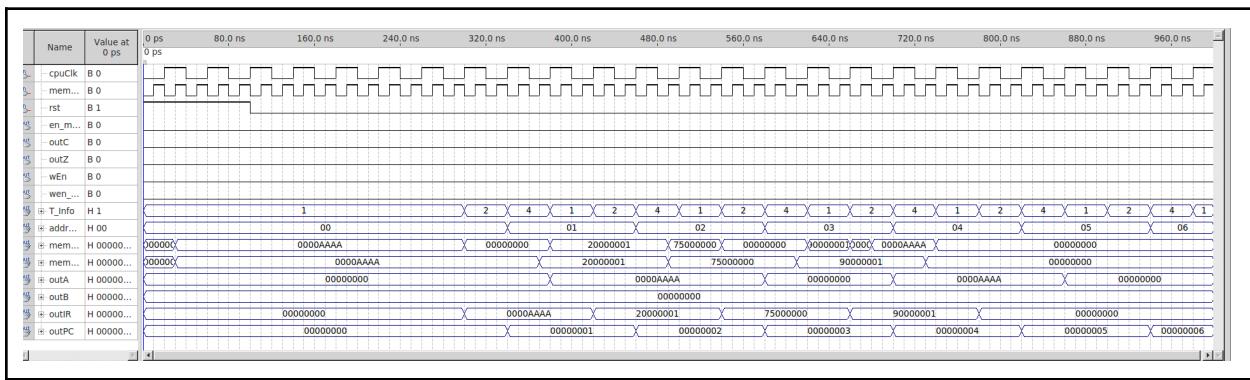


Figure 2.0: Waveform of `cpu_test_sim.vwf`

Figure 2.0 shows the general waveform for `cpu_test_sim`, which is for the starting values provided.

LDAI, STA, CLRA, LDA

Addr	+0	+1	+2	+3	+4	+5	+6	+7	+8	+9	ASCII
0	0000AAAA	20000001	75000000	90000001	00000000	00000000	00000000	00000000	00000000	00000000
10	00000000	00000000	00000000	00000000	00000000	00000000	00000000	00000000	00000000	00000000
20	00000000	00000000	00000000	00000000	00000000	00000000	00000000	00000000	00000000	00000000
30	00000000	00000000	00000000	00000000	00000000	00000000	00000000	00000000	00000000	00000000
40	00000000	00000000	00000000	00000000	00000000	00000000	00000000	00000000	00000000	00000000
50	00000000	00000000	00000000	00000000	00000000	00000000	00000000	00000000	00000000	00000000
60	00000000	00000000	00000000	00000000						

Figure 2.1.0: system_memory.mif for LDAI, STA, CLRA and LDA

Figure 2.1.0 represents what is stored for the 4 parts of the CPU. We can see that LDAI, which is Load A Immediate, is placing the value AAAA in the memory. For storing, STA we see the value 200000001 is placed. CLRA Which represents clearing A has the value 75, which will function with the CPU once the value reaches that point and LDA which is simply loading A is placed afterwards.

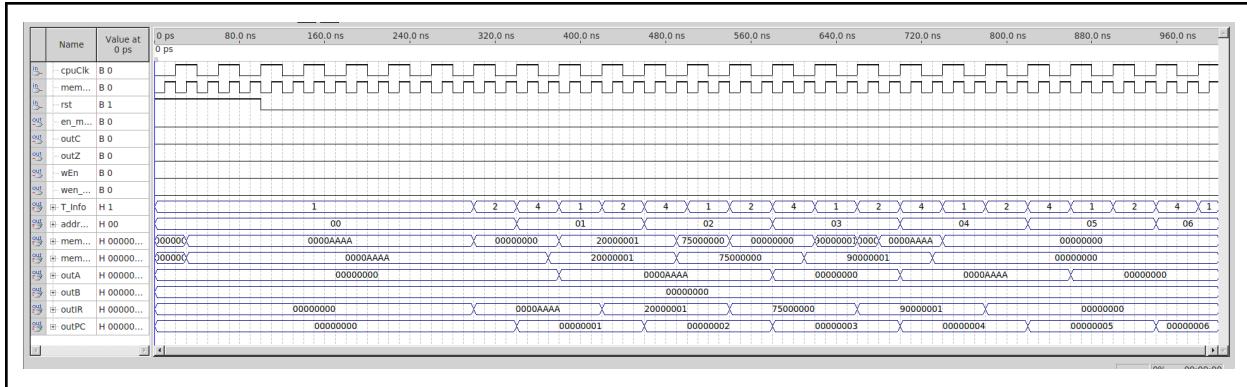


Figure 2.1.1: Waveform for LDAI, STA, CLRA, LDA

Figure 2.1.1 shows the waveform of these values. It is visible in the memory output row that the aforementioned values are all placed here. Our different outputs are representing how the values are manipulated and what we see in the outputs; for example, outA gives 0000AAAA, which is the immediately loaded A value.

LDBI, STB, CLRB, LDB

Addr	+0	+1	+2	+3	+4	+5	+6	+7	+8	+9	A
0	1000BBBB	30000001	76000000	A0000001	00000000	00000000	00000000	00000000	00000000	00000000	...
10	00000000	00000000	00000000	00000000	00000000	00000000	00000000	00000000	00000000	00000000	...
20	00000000	00000000	00000000	00000000	00000000	00000000	00000000	00000000	00000000	00000000	...
30	00000000	00000000	00000000	00000000	00000000	00000000	00000000	00000000	00000000	00000000	...
40	00000000	00000000	00000000	00000000	00000000	00000000	00000000	00000000	00000000	00000000	...
50	00000000	00000000	00000000	00000000	00000000	00000000	00000000	00000000	00000000	00000000	...
60	00000000	00000000	00000000	00000000							...

Figure 2.2.0: Memory file for LDBI, STB, CLRB, LDB

Figure 2.2.0 represents the values assigned to LDBI, which stands for Load B Immediate, STB, which stands for Store B, CLRB, which stands for Clear B, and LDB, which stands for LDB. It is visible that due to this being a B value, the values are all aligned to it in that way. So, 1000BBBB is the immediate value loaded to B, and all parts of the CPU are related to B.

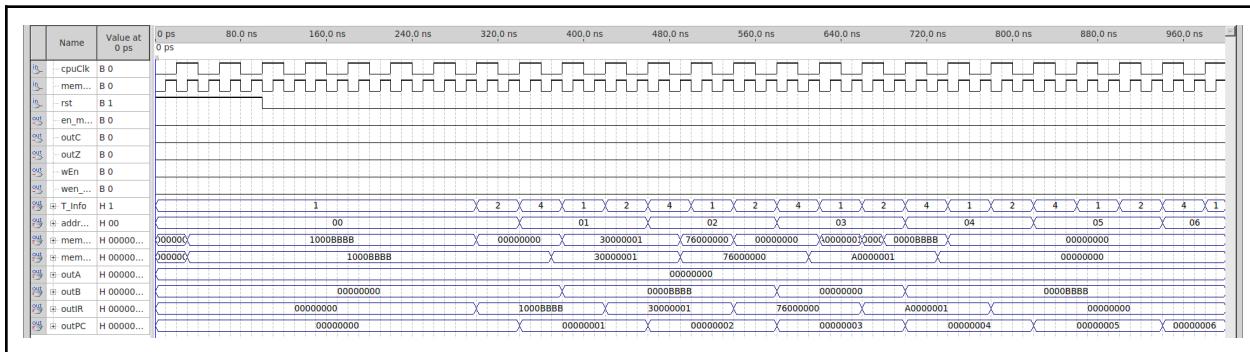


Figure 2.2.1: Waveform ofLDBI, STB, CLRB and LDB implementation

In the waveform visible in Figure 2.2.1, it is visible how the values loaded in the memory are placed. After going through the system, the outA output remains 0, as it is not interacted with. Instead, outB is implemented and has values that result from the B values travelling through.

LUI: Load Upper Immediate

Addr	+0	+1	+2	+3	+4	+5	+6	+7	+8	+9	/
0	4000AAAA	00000000	00000000	00000000	00000000	00000000	00000000	00000000	00000000	00000000	...
10	00000000	00000000	00000000	00000000	00000000	00000000	00000000	00000000	00000000	00000000	...
20	00000000	00000000	00000000	00000000	00000000	00000000	00000000	00000000	00000000	00000000	...
30	00000000	00000000	00000000	00000000	00000000	00000000	00000000	00000000	00000000	00000000	...
40	00000000	00000000	00000000	00000000	00000000	00000000	00000000	00000000	00000000	00000000	...
50	00000000	00000000	00000000	00000000	00000000	00000000	00000000	00000000	00000000	00000000	...
60	00000000	00000000	00000000	00000000	00000000	00000000	00000000	00000000	00000000	00000000	...

Figure 2.3.0: Memory file of LUI

Figure 2.3.0 Represents the value assigned to LUI, or Load Upper Immediate. The value, 4000AAAA, shows how in the upper 16 bits, a value is loaded. As for the AAAA is a repeating set of values.

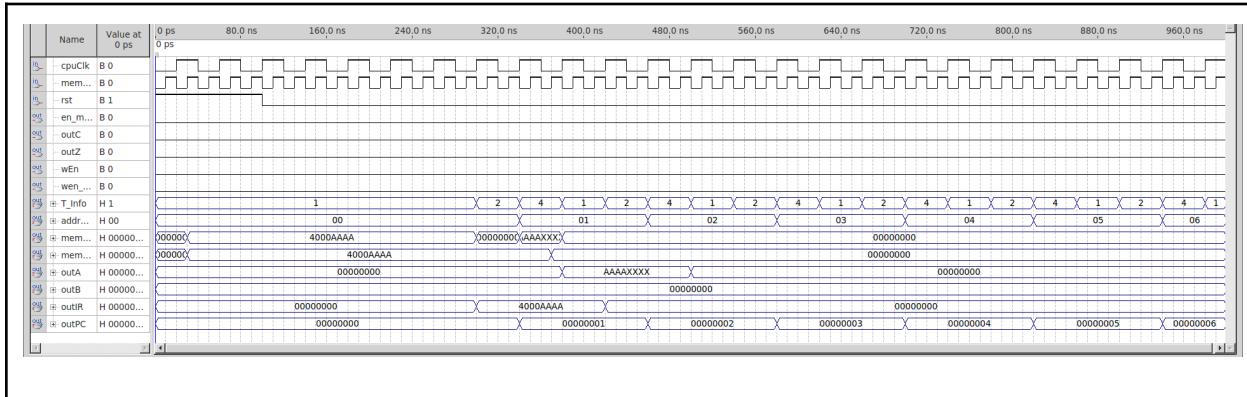


Figure 2.3.1: Waveform of LUI implementation

Figure 2.3.1 shows the implementation of the LUI function. It is visible by looking at the outputs, that in outIR, the value 4000AAAA is loaded immediately after a few moments, and the remaining values are all 0. This shows that it has been successfully implemented.

JMP: Jump

Addr	+0	+1	+2	+3	+4	+5	+6	+7	+8	+9	ASCII
0	5000AAAA	00000000	00000000	00000000	00000000	00000000	00000000	00000000	00000000	00000000
10	00000000	00000000	00000000	00000000	00000000	00000000	00000000	00000000	00000000	00000000
20	00000000	00000000	00000000	00000000	00000000	00000000	00000000	00000000	00000000	00000000
30	00000000	00000000	00000000	00000000	00000000	00000000	00000000	00000000	00000000	00000000
40	00000000	00000000	00000000	00000000	00000000	00000000	00000000	00000000	00000000	00000000
50	00000000	00000000	00000000	00000000	00000000	00000000	00000000	00000000	00000000	00000000
60	00000000	00000000	00000000	00000000	00000000	00000000	00000000	00000000	00000000	00000000

Figure 2.4.0: Memory file of JMP

This file represents the value assigned to Jump, which allows going from one place in the memory to another.

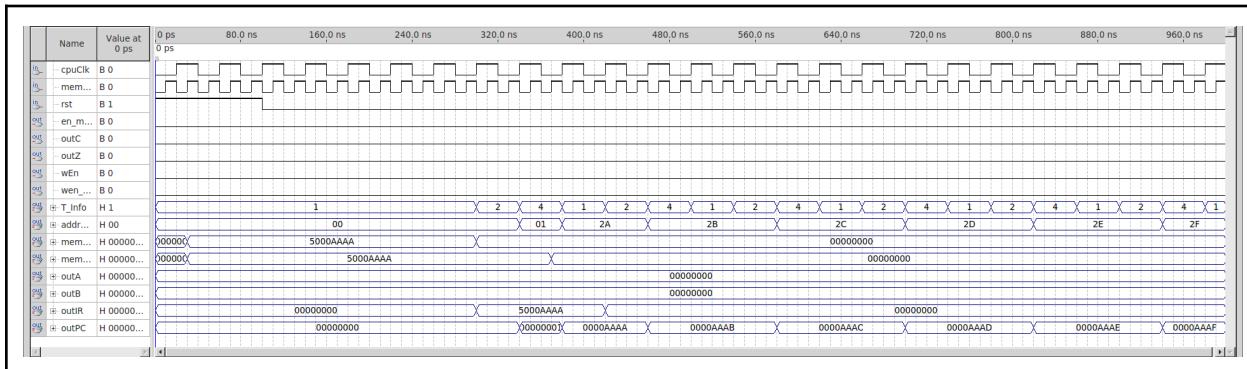


Figure 2.4.1: Waveform of JMP implementation in CPU

Figure 2.4.1 shows how JMP, or Jump is implemented. It is visible by looking at the memory of how the actual jump exists, and the T_info 1 value exists first in a certain timeframe at the beginning. However, in outPC, it is visible that by jumping, the 1 value now exists at a later point of the clock in a different address.

ANDI: AND Immediate

Addr	+0	+1	+2	+3	+4	+5	+6	+7	+8	+9	ASCII
0	00000006	7900000B	00000000	00000000	00000000	00000000	00000000	00000000	00000000	00000000
10	00000000	00000000	00000000	00000000	00000000	00000000	00000000	00000000	00000000	00000000
20	00000000	00000000	00000000	00000000	00000000	00000000	00000000	00000000	00000000	00000000
30	00000000	00000000	00000000	00000000	00000000	00000000	00000000	00000000	00000000	00000000
40	00000000	00000000	00000000	00000000	00000000	00000000	00000000	00000000	00000000	00000000
50	00000000	00000000	00000000	00000000	00000000	00000000	00000000	00000000	00000000	00000000
60	00000000	00000000	00000000	00000000	00000000	00000000	00000000	00000000	00000000	00000000

Figure 2.5.0: Memory File of AND Immediate

Figure 2.5.0 represents the value for ANDI, which covers two spaces. One that has values only in the last 4 bits, and one that covers the first 8 bits and then the last 4.

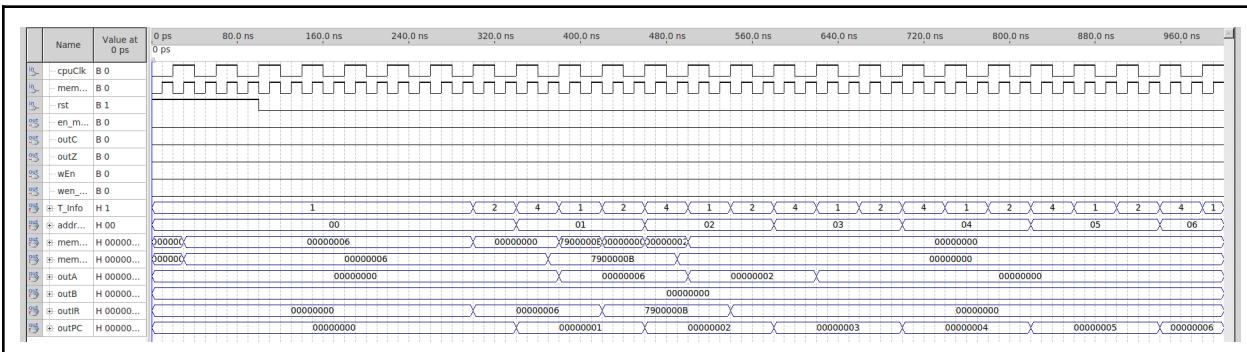


Figure 2.5.1: Waveform of ANDI CPU implementation

In Figure 2.5.1, it is visible that the two values allow for producing the AND of two values that are inserted.

ADDI: Add Immediate

Addr	+0	+1	+2	+3	+4	+5	+6	+7	+8	+9	ASCII
0	00000006	7100000B	00000000	00000000	00000000	00000000	00000000	00000000	00000000	00000000
10	00000000	00000000	00000000	00000000	00000000	00000000	00000000	00000000	00000000	00000000
20	00000000	00000000	00000000	00000000	00000000	00000000	00000000	00000000	00000000	00000000
30	00000000	00000000	00000000	00000000	00000000	00000000	00000000	00000000	00000000	00000000
40	00000000	00000000	00000000	00000000	00000000	00000000	00000000	00000000	00000000	00000000
50	00000000	00000000	00000000	00000000	00000000	00000000	00000000	00000000	00000000	00000000
60	00000000	00000000	00000000	00000000	00000000	00000000	00000000	00000000	00000000	00000000

Figure 2.6.0: Memory File of ADDI Add Immediate

This file shows how the value exists and is immediately added to in memory with another value.

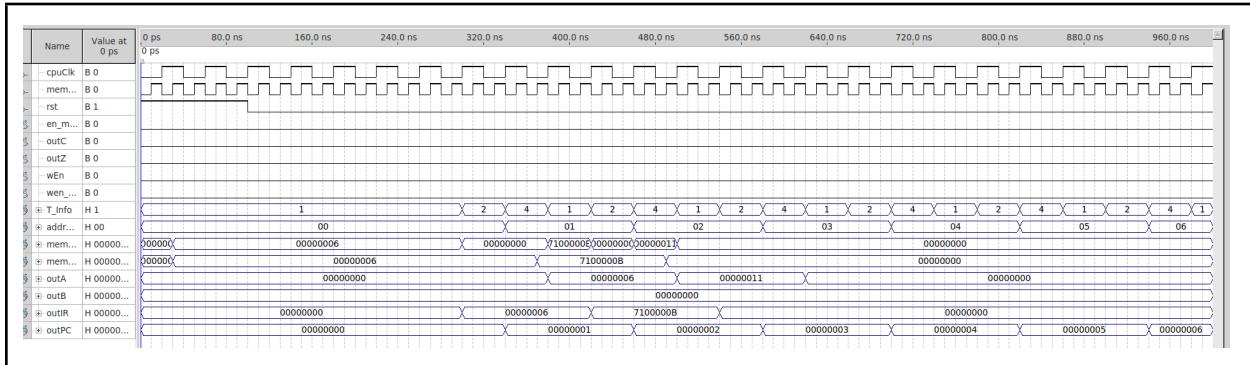


Figure 2.6.1: Waveform of ADDI Add Immediate

Figure 2.6.1 represents how given an input value, it can be added to a constant value as soon as it enters a certain time frame. If the memory row is observed, which is the actual ADDI implementation, the final output shows how the value has been added to.

ORI: Or Immediate

Addr	+0	+1	+2	+3	+4	+5	+6	+7	+8	+9	ASCII
0	00000006	7D00000B	00000000	00000000	00000000	00000000	00000000	00000000	00000000	00000000
10	00000000	00000000	00000000	00000000	00000000	00000000	00000000	00000000	00000000	00000000
20	00000000	00000000	00000000	00000000	00000000	00000000	00000000	00000000	00000000	00000000
30	00000000	00000000	00000000	00000000	00000000	00000000	00000000	00000000	00000000	00000000
40	00000000	00000000	00000000	00000000	00000000	00000000	00000000	00000000	00000000	00000000
50	00000000	00000000	00000000	00000000	00000000	00000000	00000000	00000000	00000000	00000000
60	00000000	00000000	00000000	00000000	00000000	00000000	00000000	00000000	00000000	00000000

Figure 2.7.0: Memory Value For ORI Or Immediate

The memory values for Or Immediate consist of two, one being the actual OR function (represented as 0006) and the other being the immediate value to be added.

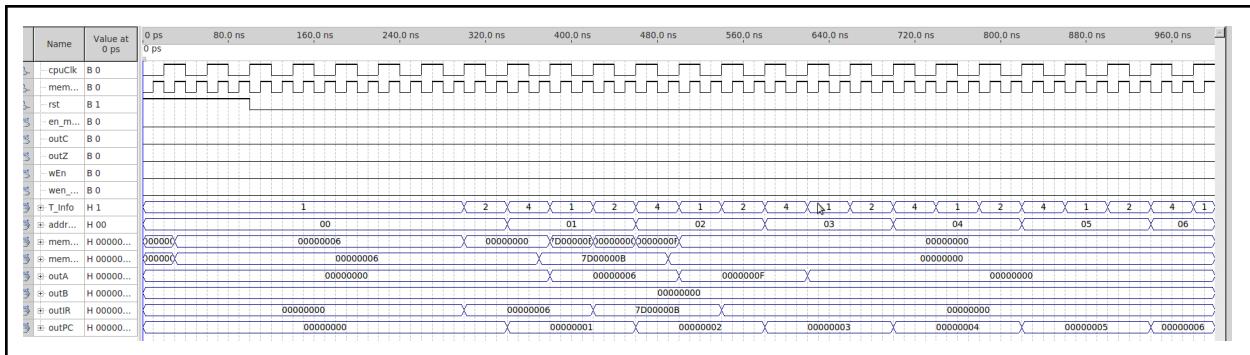


Figure 2.7.1: Waveform of ORI OR Immediate CPU Implementation

Figure 2.7.1 Shows the actual CPU Implementation of ORI. The memory holds the actual OR function, which is visibly output in the outA row. The value is successfully OR'd with another value.

ADD: Addition

Addr	+0	+1	+2	+3	+4	+5	+6	+7	+8	+9	ASCII
0	00000005	10000003	70000000	00000000	00000000	00000000	00000000	00000000	00000000	00000000
10	00000000	00000000	00000000	00000000	00000000	00000000	00000000	00000000	00000000	00000000
20	00000000	00000000	00000000	00000000	00000000	00000000	00000000	00000000	00000000	00000000
30	00000000	00000000	00000000	00000000	00000000	00000000	00000000	00000000	00000000	00000000
40	00000000	00000000	00000000	00000000	00000000	00000000	00000000	00000000	00000000	00000000
50	00000000	00000000	00000000	00000000	00000000	00000000	00000000	00000000	00000000	00000000
60	00000000	00000000	00000000	00000000	00000000	00000000	00000000	00000000	00000000	00000000

Figure 2.8.0: Memory File of ADD (Addition)

This memory file represents the addition function, which is represented by the space under +2. The other two values visible are there since in order to add, it is necessary for two values to exist.

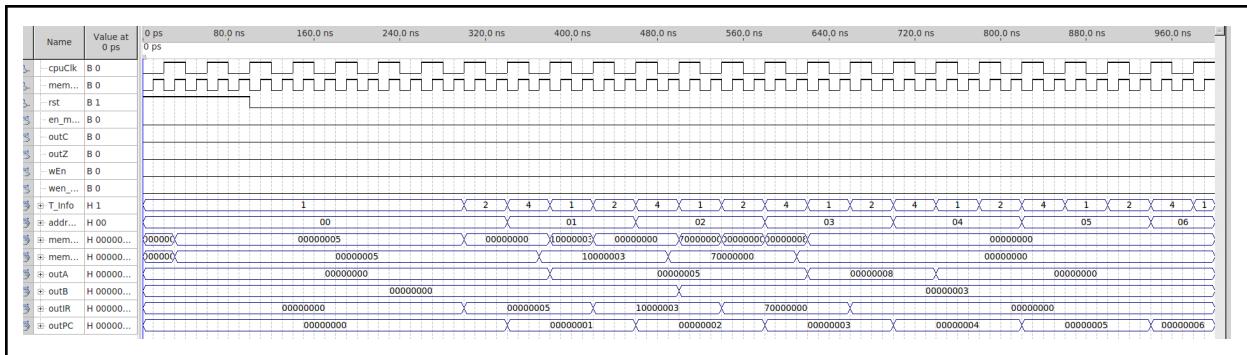


Figure 2.8.1: Waveform of ADD

Figure 2.8.1 represents the waveform that consists of ADD. It is visible that in memory, we have our two values that are to be added. Implemented by the add function, in outIR we can see that the two values are added to provide the final value.

SUB: Subtract

Addr	+0	+1	+2	+3	+4	+5	+6	+7	+8	+9	ASCII
0	00000005	10000003	72000000	00000000	00000000	00000000	00000000	00000000	00000000	00000000
10	00000000	00000000	00000000	00000000	00000000	00000000	00000000	00000000	00000000	00000000
20	00000000	00000000	00000000	00000000	00000000	00000000	00000000	00000000	00000000	00000000
30	00000000	00000000	00000000	00000000	00000000	00000000	00000000	00000000	00000000	00000000
40	00000000	00000000	00000000	00000000	00000000	00000000	00000000	00000000	00000000	00000000
50	00000000	00000000	00000000	00000000	00000000	00000000	00000000	00000000	00000000	00000000
60	00000000	00000000	00000000	00000000	00000000	00000000	00000000	00000000	00000000	00000000

Figure 2.9.0: Memory File for Subtract (SUB)

This memory file is similar to ADD, with the main difference being that the SUB is now implemented, having a value of 72 instead of 70. The values move on to be subtracted.

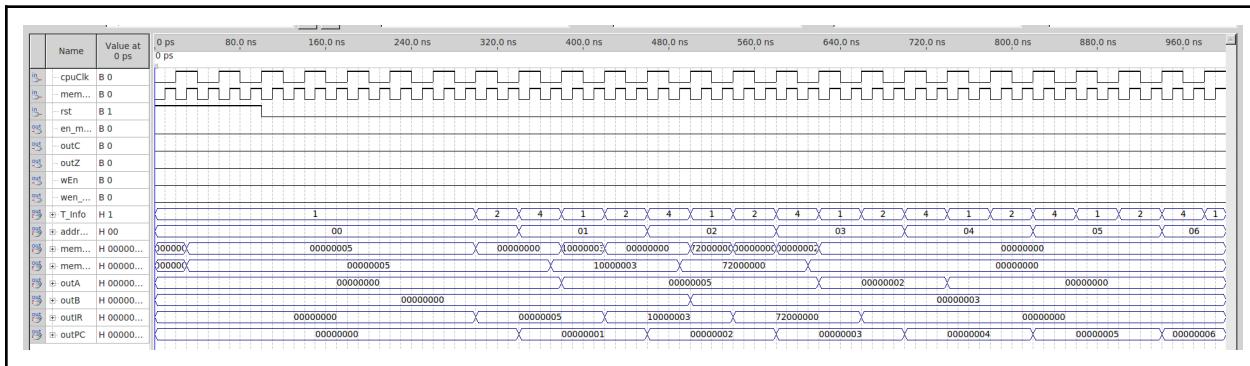


Figure 2.9.1: Waveform of SUB implementation on CPU

Figure 2.9.1 Shows the waveform of the SUB implementation on the CPU. It is once again visible to see how the values are implemented through the outA section, where we can see that 5 and 3 are subtracted to give us 2.

DECA: Decrement A

Addr	+0	+1	+2	+3	+4	+5	+6	+7	+8	+9	ASCII
0	0000AAAA	7E000000	70000000	00000000	00000000	00000000	00000000	00000000	00000000	00000000
10	00000000	00000000	00000000	00000000	00000000	00000000	00000000	00000000	00000000	00000000
20	00000000	00000000	00000000	00000000	00000000	00000000	00000000	00000000	00000000	00000000
30	00000000	00000000	00000000	00000000	00000000	00000000	00000000	00000000	00000000	00000000
40	00000000	00000000	00000000	00000000	00000000	00000000	00000000	00000000	00000000	00000000
50	00000000	00000000	00000000	00000000	00000000	00000000	00000000	00000000	00000000	00000000
60	00000000	00000000	00000000	00000000							...

Figure 2.10.0: Memory File of DECA (Decrement A)

This memory file shows the Decrementing of A. +0 represents the A possible A values (AAAA), and goes on to decrement the value by 1.

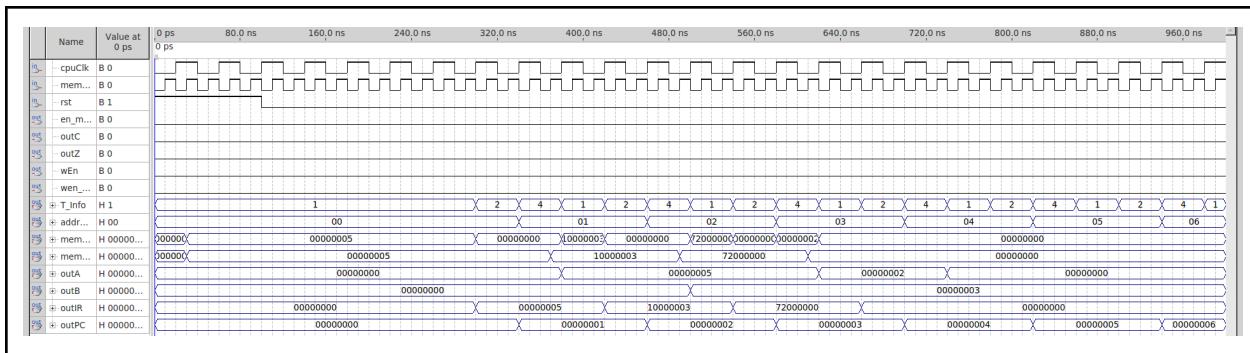


Figure 2.10.1: Waveform of DECA implementation on CPU

Figure 2.10.1 represents the decrementing of the values, whose output is visible in outA. With the initial value existing, the final output value is now one less, which shows that it has successfully been decremented.

INCA: Increment A

Addr	+0	+1	+2	+3	+4	+5	+6	+7	+8	+9	ASCII
0	0000AAAA	73000000	70000000	00000000	00000000	00000000	00000000	00000000	00000000	00000000
10	00000000	00000000	00000000	00000000	00000000	00000000	00000000	00000000	00000000	00000000
20	00000000	00000000	00000000	00000000	00000000	00000000	00000000	00000000	00000000	00000000
30	00000000	00000000	00000000	00000000	00000000	00000000	00000000	00000000	00000000	00000000
40	00000000	00000000	00000000	00000000	00000000	00000000	00000000	00000000	00000000	00000000
50	00000000	00000000	00000000	00000000	00000000	00000000	00000000	00000000	00000000	00000000
60	00000000	00000000	00000000	00000000						

Figure 2.11.0: Memory File of Increment A (INCA)

The main difference between DECA and INCA lies in the +1 space, which changes the second 4 bits to allow for incrementing by one (or adding one). As it is still A that is being incremented, the +0 value remains as AAAA for the last 16 bits.

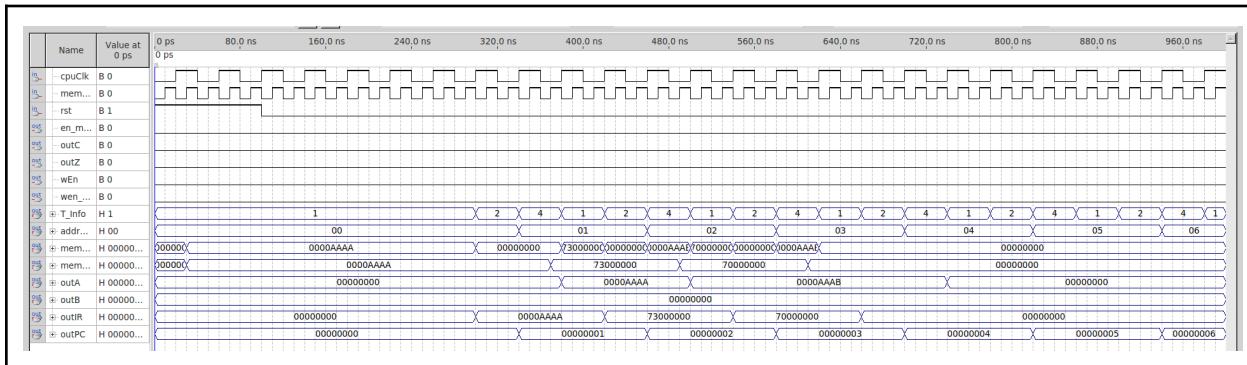


Figure 2.11.1: Waveform of Increment A (INCA)

Figure 2.11.1 Shows the incrementing of the value loaded into A. What begins as AAAA can be seen in outA as changing to AAAB, which shows that the last 4 bits have been incremented and changed the value from A to the next one, which is B.

ROL: Rotate Left

Addr	+0	+1	+2	+3	+4	+5	+6	+7	+8	+9	ASCII
0	00000008	74000000	70000000	00000000	00000000	00000000	00000000	00000000	00000000	00000000
10	00000000	00000000	00000000	00000000	00000000	00000000	00000000	00000000	00000000	00000000
20	00000000	00000000	00000000	00000000	00000000	00000000	00000000	00000000	00000000	00000000
30	00000000	00000000	00000000	00000000	00000000	00000000	00000000	00000000	00000000	00000000
40	00000000	00000000	00000000	00000000	00000000	00000000	00000000	00000000	00000000	00000000
50	00000000	00000000	00000000	00000000	00000000	00000000	00000000	00000000	00000000	00000000
60	00000000	00000000	00000000	00000000	00000000	00000000	00000000	00000000	00000000	00000000

Figure 2.12.0: Memory File for Rotate Left (ROL)

The memory file for ROL allows for shifting the bits in the existing value to the left by one.

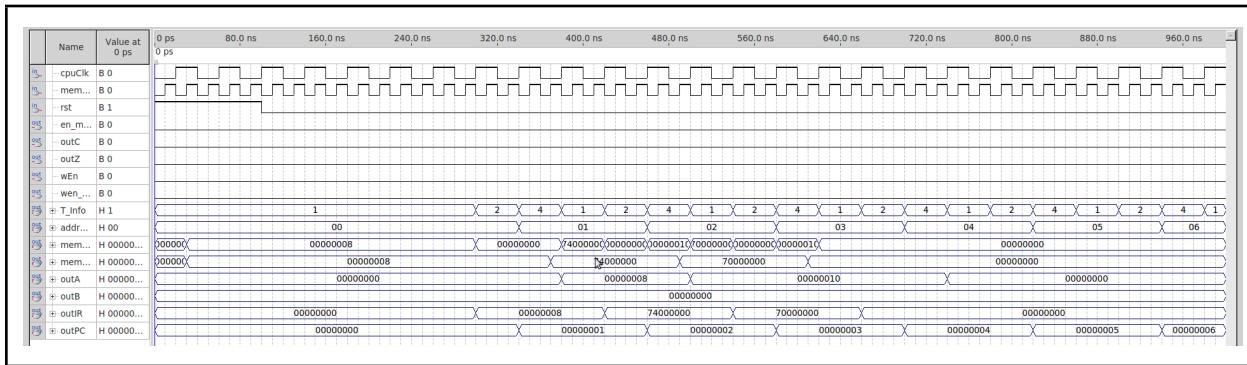


Figure 2.12.1: Waveform of Rotate Left ROL

Figure 2.12.1 represents how the values implemented are shifted to the left. If the outA section is observed, it is visible how the value has gone from 00000001 to 00000000, showing that it has successfully been shifted.

ROR: Rotate Right

Addr	+0	+1	+2	+3	+4	+5	+6	+7	+8	+9	ASCII
0	00000008	7F000000	70000000	00000000	00000000	00000000	00000000	00000000	00000000	00000000
10	00000000	00000000	00000000	00000000	00000000	00000000	00000000	00000000	00000000	00000000
20	00000000	00000000	00000000	00000000	00000000	00000000	00000000	00000000	00000000	00000000
30	00000000	00000000	00000000	00000000	00000000	00000000	00000000	00000000	00000000	00000000
40	00000000	00000000	00000000	00000000	00000000	00000000	00000000	00000000	00000000	00000000
50	00000000	00000000	00000000	00000000	00000000	00000000	00000000	00000000	00000000	00000000
60	00000000	00000000	00000000	00000000	00000000	00000000	00000000	00000000	00000000	00000000

Figure 2.13.0: Memory File for Rotate Right (ROR)

The memory file for ROR represents how the implemented value would be shifted right by one bit.

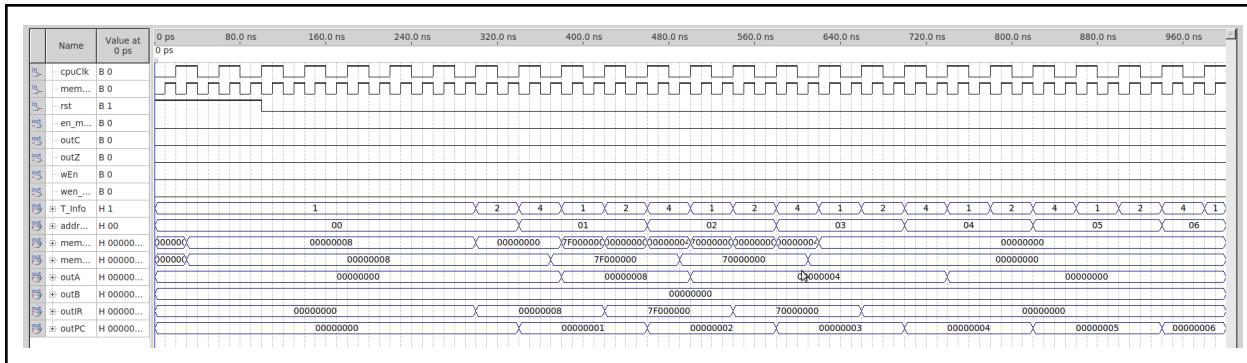


Figure 2.13.1: Waveform of Rotate Right (ROR) Implemented on the CPU

In this waveform, it is important to observe the rows for memory and for outA. With the initial given values, it is shifted one bit towards the right, representing it with an output of 0004 for the last 4 bits.

BEQ: Branch If Equal

Addr	+0	+1	+2	+3	+4	+5	+6	+7	+8	+9	ASCII
0	0000AAAA	1000AAAA	600000F0	00000000	00000000	00000000	00000000	00000000	00000000	00000000
10	00000000	00000000	00000000	00000000	00000000	00000000	00000000	00000000	00000000	00000000
20	00000000	00000000	00000000	00000000	00000000	00000000	00000000	00000000	00000000	00000000
30	00000000	00000000	00000000	00000000	00000000	00000000	00000000	00000000	00000000	00000000
40	00000000	00000000	00000000	00000000	00000000	00000000	00000000	00000000	00000000	00000000
50	00000000	00000000	00000000	00000000	00000000	00000000	00000000	00000000	00000000	00000000
60	00000000	00000000	00000000	00000000							...

Figure 2.14.0: Memory File for Branch If Equal (BEQ)

For this section, we are focusing on AAAA. There are two steps for this process. First, two values are compared to each other and determined if they are equal or not. If they are indeed equal, branching is then applied.

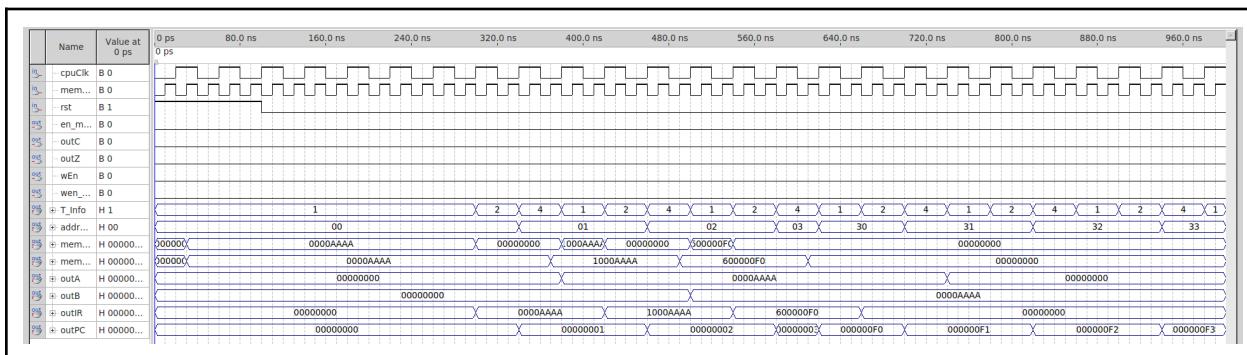


Figure 2.14.1: Waveform of Branch If Equal (BEQ)

In this waveform, we can see that the two values that we would be looking at are in AAAA. The system has AAAA followed by 1000AAAA; since we want to know if it's equal, we can compare outA and outB.

At a certain point in the time, it is visible that both have 0000AAAA, which is specifically where it is confirmed they are equal. In that specific space, we can see that outIR changes to 600000F0, and outPC also changes, showing that it is successfully branched.

BNE: Branch If Not Equal

Addr	+0	+1	+2	+3	+4	+5	+6	+7	+8	+9	ASCII
0	0000AAAA	1000BBBB	800000F0	00000000	00000000	00000000	00000000	00000000	00000000	00000000
10	00000000	00000000	00000000	00000000	00000000	00000000	00000000	00000000	00000000	00000000
20	00000000	00000000	00000000	00000000	00000000	00000000	00000000	00000000	00000000	00000000
30	00000000	00000000	00000000	00000000	00000000	00000000	00000000	00000000	00000000	00000000
40	00000000	00000000	00000000	00000000	00000000	00000000	00000000	00000000	00000000	00000000
50	00000000	00000000	00000000	00000000	00000000	00000000	00000000	00000000	00000000	00000000
60	00000000	00000000	00000000	00000000						

Figure 2.15.0: Memory File of Branch If Not Equal (BNE)

This memory file is representing how branching would occur if it is not equal. We are comparing the values in +0, and in the case that it is not equal it would branch, represented by 1000BBBB.

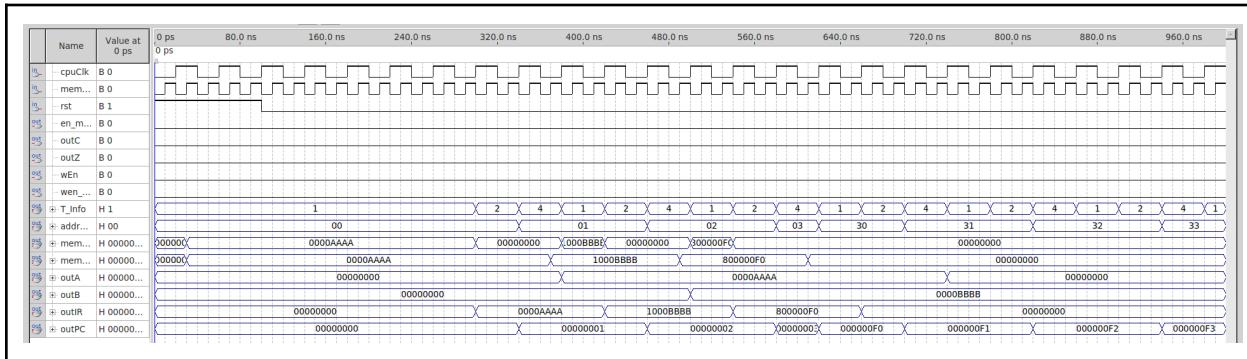


Figure 2.15.1: Waveform of Branch If Not Equal (BNE)

In this waveform, it is visible how as the timing goes onwards, the comparisons are made. We can see here that for outA and outB, for a good part of the beginning they are first both 00000000. However, after a certain point, we see that outA has 0000AAAA, while outB has 0000BBBB. Here, we are implementing branch if not equal, which is then done and visible in both outIR and outPC, as the values go from incrementing in outPC by one, to F0, showing that a branch has been done.